

M R

Ahmed Mahdy



مدرس خصوصي

حضورى

اونلاين

يحصل الطالب علي

مقاطع فيديو هات لشرح المقرر بشكل وافي

ملخص للمادة Pdf للمذكرة واطراجة

محاضرات مباشرة علي برنامج زووم

مناقشة الأجزاء الغير مفهومة

تواصل مستمر مع معلم المادة


للتواصل

0567630097

0565657741




BASIC CIRCUIT ANALYSIS

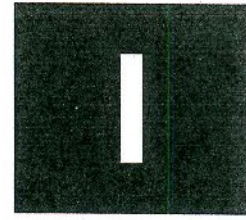

- 1 Basic DC Circuits
- 2 General DC Circuit Analysis
- 3 Transient Circuits


تيار مستقیم
Direct Current
D.C

DC Voltage

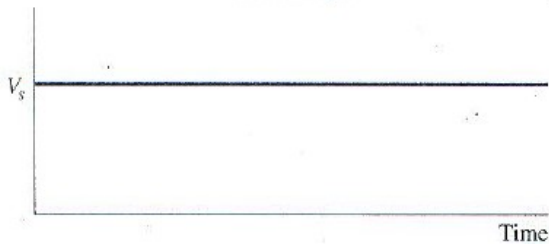

تيار متناوب
alternating current
A.C

AC Voltage

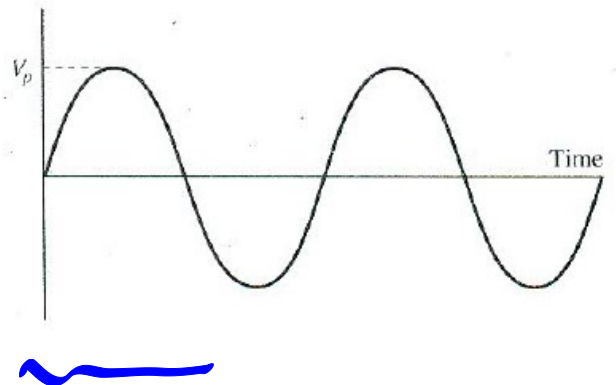

Units and Prefixes

We will introduce many units throughout the text for describing the values of various electrical variables and components. Table 1-1 shows a compilation of some of the most basic

Table 1-1 Basic electric variables used in dc circuit analysis.

Variable	Symbol	Unit	Unit Abbreviation
Time	t	second	s
Charge	Q	coulomb	C
Current	I	ampere	A
Voltage	V (or E)	volt	V
Energy	W	joule	J
Power	P	watt	W
Resistance	R	ohm	Ω
Conductance	G	siemens	S

Table 1-2 Prefixes in SI units.

Value	Prefix	Abbreviation
10^{-12}	pico	p
10^{-9}	nano	n
10^{-6}	micro	μ
10^{-3}	milli	m
10^3	kilo	k
10^6	mega	M
10^9	giga	G



$$R = 1000 \Omega = 1 \text{ k}\Omega$$

$$V = 0.005 \text{ V} = 5 \text{ mV}$$

ideal sources

independent
مستقل

dependent
غير مستقل

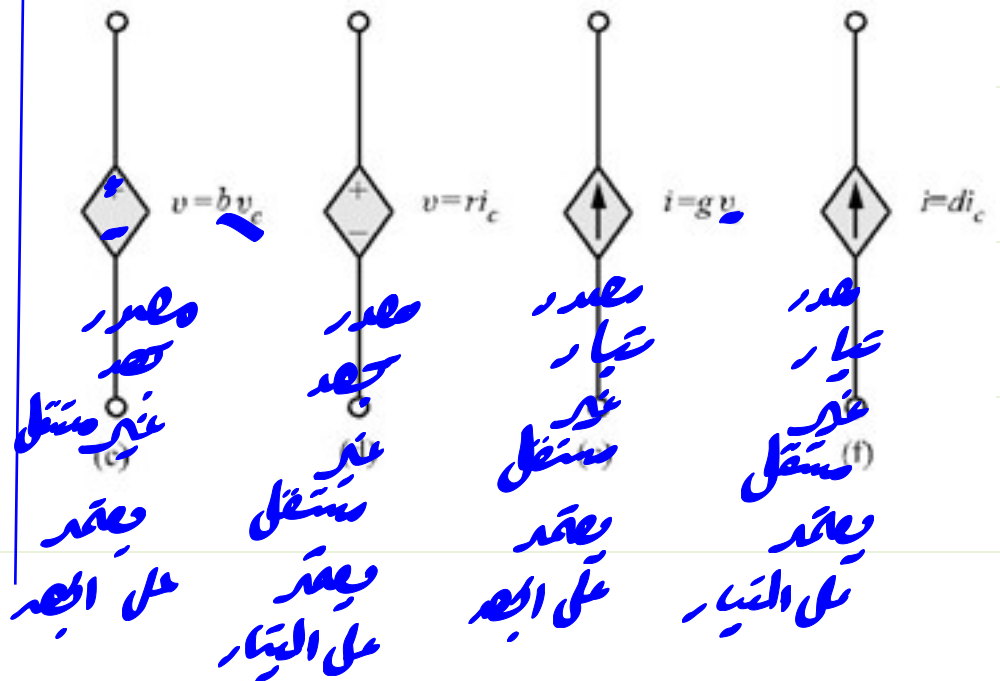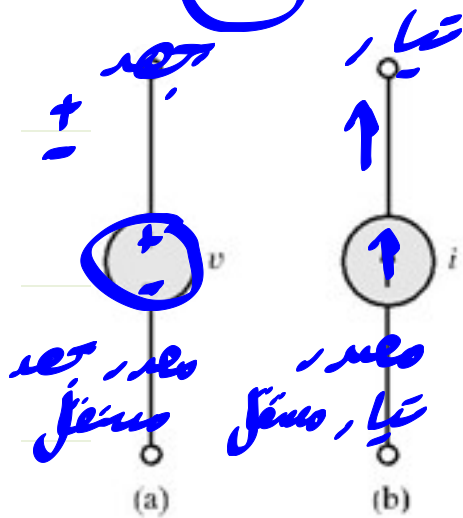

قانون اوم Ohm's law

$$\frac{I}{1} = \frac{V}{R}$$

القدرة Power

$$P = I \cdot V \rightarrow ①$$

$$P = \frac{V}{R} \cdot V = \frac{V^2}{R} \rightarrow ②$$


$$P = I (IR) = I^2 R \rightarrow ③$$

EXAMPLE 1-1

A simple circuit of the form shown in Figure 1-8(b) has $V = 12\text{ V}$ and $R = 4.7\text{ k}\Omega$. Determine the current I .

$$V = 12\text{ V}$$

$$R = 4.7 \times 1000\ \Omega$$

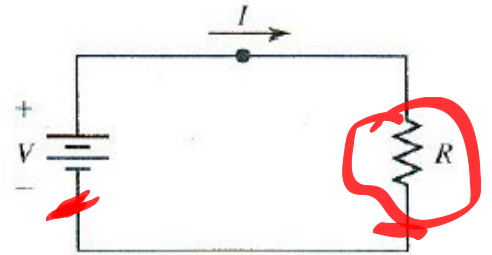

(b)

$$I = \frac{V}{R} = \frac{12}{4.7 \times 1000} = \underline{0.0025\text{ A}}$$

$$= 2.5 \times 10^{-3}\text{ A} = \underline{2.5\text{ mA}}$$

EXAMPLE 1-2

For the simple circuit of Example 1-1, determine the power delivered by the source and the power dissipated by the resistance.

Chose unit!

$$P = I \cdot V = 2.5 \times 10^{-3} \times 12 = \underline{30.658\text{ mW}}$$

$$\frac{V^2}{R}$$

$$I^2 R$$

EXAMPLE 1-3

The output current of a certain integrated circuit is $\overset{I}{6\text{ mA}}$ and it is flowing into a resistance of value $5\text{ k}\Omega$. Determine the voltage across the resistance.

$$I = 6 \times 10^{-3}\text{ A}, R = 5 \times 10^3\ \Omega$$

$$I = \frac{V}{R} \Rightarrow V = IR = 6 \times 10^{-3} \times 5 \times 10^3$$

$$V = 30\text{ V}$$

EXAMPLE 1-4

Determine the "hot" resistance of a 60-W bulb operated from an ac effective voltage of 120 V.

$$P = 60 \text{ W} , V = 120 \text{ V}$$

$$I = \frac{V}{R} \quad \times$$

$$P = I \cdot V = \frac{V^2}{R} = \underline{I^2 R}$$

$$P = \frac{V^2}{R}$$

$$\underline{60} = \frac{120^2}{R} \Rightarrow R = \frac{120^2}{\underline{60}} = 240 \, \Omega$$

EXAMPLE 1-5

The power dissipated in a certain resistance is 100 W and the current is 4 A. Determine the resistance.

$$P = I^2 R$$

$$100 = 16 R \Rightarrow R = 6.25 \, \Omega$$

EXAMPLE 1-6

We determine the resistance of a device under operating conditions by measuring the voltage across the device and the current through it. The voltmeter reads 120.0 V and the ammeter reads 2.012 A. Determine the resistance.

$$I = \frac{V}{R} \Rightarrow R = \frac{V}{I} = \frac{120}{2.012} = 59.64 \, \Omega$$