

M R

Ahmed Mahdy



مدرس خصوصي

حضورى

اونلاين

محصل الطالب علي

مقاطع فيديو هات لشرح المقرر بشكل وافى

ملخص للمادة Pdf للمذكرة واطراجة

محاضرات مباشرة علي برنامج زووم

مناقشة الأجزاء الغير مفهومة

تواصل مستمر مع معلم المادة

للتواصل

0567630097

0565657741

استاتيكا	فيزياء
الكترونيا	دوائر كهربية
هيدروليكا	ميكانيكا الانشآت




1-7 Single-Loop or Series Circuit

mesh

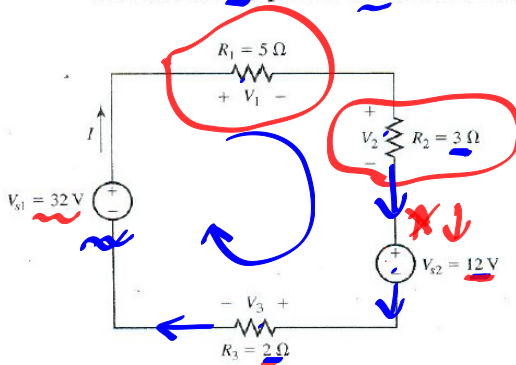EXAMPLE 1-11

For the circuit of Figure 1-24, determine (a) loop current, (b) voltages across all resistances, and (c) power delivered or absorbed by each component in the circuit.



Handwritten notes:

$$I = \frac{V}{R} = \frac{32}{8} = 4$$

$$V_1 = 5 \times 2 = 10$$

$$I = \frac{V_2}{R_2} = \frac{6}{3} = 2$$

FIGURE 1-24 Circuit of Example 1-11.

15. v, l

$$-32 + V_1 + V_2 + 12 + V_3 = 0$$

$5I \quad 3I \quad 2I$

$$-32 + 5I + 3I + 12 + 2I = 0$$

$$\frac{10I}{10} = \frac{20}{10} \Rightarrow I = 2A$$

$V_1 = 10V$ / $V_2 = 6V$ - $V_3 = 4V$

$I \cdot V \quad \frac{V^2}{R} = I^2 R$

$P_{s1} = 2 \times 32 = 64W$

$P_1 = 2 \times 10 = 20W$


$P_2 = 4 \times 3 = 12W$

$P_{s2} = 2 \times 12W$

$P_3 = \frac{4^2}{2} = 8W$


Variable	Power delivered	Power absorbed
V_{s1}	64	
V_1		20
V_2		12
V_{s2}		24
V_3		8

64w / 64w

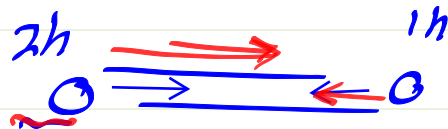

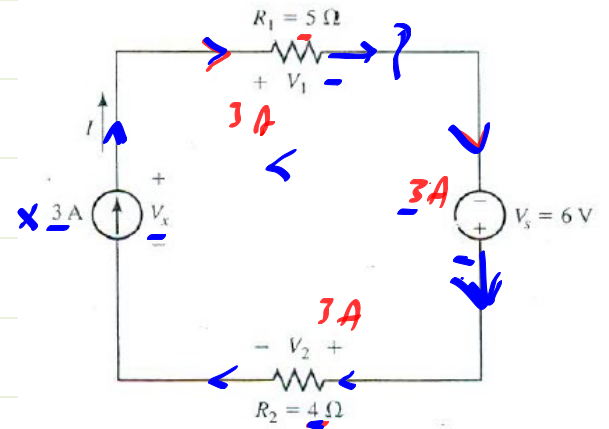EXAMPLE 1-12

For the circuit of Figure 1-25, determine (a) loop current, (b) voltages across all resistances, (c) voltage across the current source, and (d) power delivered or absorbed by each component in circuit.



$$I = 3 \text{ A}$$

$$V = IR$$

$$-V_x + V_1 - V_2 + 6 = 0$$

$$-15 + V_x - 12 + 6 = 0$$

$$V_x = 21 \text{ V}$$

$$V_1 = IR_1 = 3 \times 5 = 15 \text{ V}$$

$$V_2 = 12 \text{ V}$$

$$P_x = I \cdot V = 3 \times 21 = 63 \text{ W}$$

$$P_1 = 3 \times 15 = 45 \text{ W}$$

$$P_s = 18 \text{ W}$$


$$P_2 = 3 \times 12 = 36 \text{ W}$$

Variable	Power delivered	Power absorbed
V_x	63	
V_1		45
V_s	18	
V_2		36
	81 W	81 W

$$2h \quad \bigcirc \rightarrow \quad \bigcirc \rightarrow 1h$$

loop-mesh

1-8 Single Node-Pair or Parallel Circuit

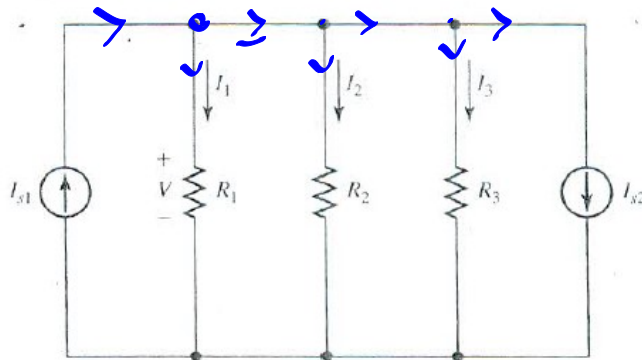

EXAMPLE 1-13

For the circuit of Figure 1-28, determine (a) voltage across the circuit, (b) currents through the three resistances, (c) current through voltage source, and (d) all values of power delivered and power absorbed.

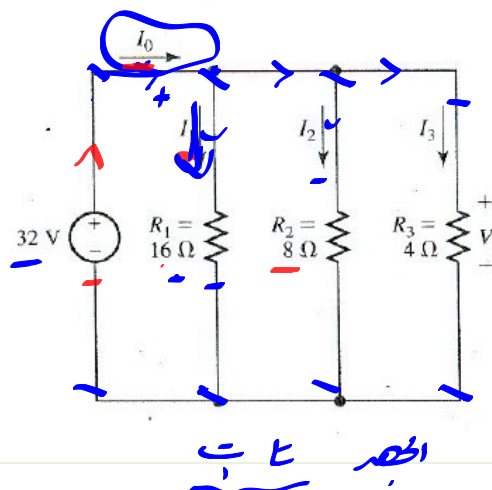


FIGURE 1-28
Circuit of Example 1-13.

$$V = 32V$$

$$I_0 = I_1 + I_2 + I_3$$

$$I_0 = 2 + 4 + 8 = 14A$$

$$I_1 = \frac{V}{R_1} = \frac{32}{16} = 2A$$

$$I_2 = \frac{V}{R_2} = \frac{32}{8} = 4A$$

$$I_3 = \frac{32}{4} = 8A$$

$$P = I \cdot V = V^2 R = I^2 R$$

$$2^2 \times 16$$

$$4^2 \times 8$$

$$8^2 \times 4$$

Variable	Power delivered	Power absorbed
V	448	
R ₁		64
R ₂		128
R ₃		256
		<u>448w</u>

EXAMPLE 1-14

For the circuit of Figure 1-29, determine (a) voltage across the node pair, (b) current through each of the resistances, and (c) all values of power delivered and absorbed.

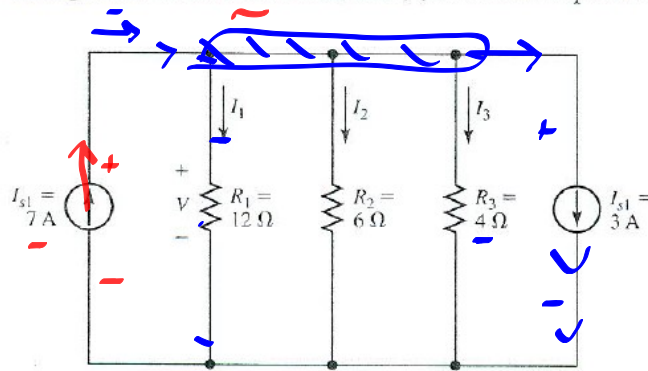


FIGURE 1-29
Circuit of Example 1-14.

15. C. Q

$$7 = I_1 + I_2 + I_3 + 3 = 0$$

$$\frac{V}{12} + \frac{2V}{6} + \frac{3V}{4} = 4 \Rightarrow 8V = 48 + 4V$$

$$V = 8V$$

$$I_1 = \frac{V}{R_1} = \frac{8}{12} = 0.67A$$

$$I_2 = \frac{V}{R_2} = \frac{8}{6} = 1.33$$

$$I_3 = \frac{V}{R_3} = \frac{8}{4} = 2A$$

$$7 \neq 8$$

$$0.67^2 \times 12$$

$$1.33^2 \times 6$$

$$I^2 R = I \cdot V = 3 \times 8$$

Variable	Power delivered	Power absorbed
I_{s1}	56W	
R_1		5.79
R_2		10.6
R_3		16
I_{s2}		24
	56	56W

1-9 Voltage and Current Divider Rules

