

MR

Ahmed Mahdy



مدرس خصوصي

حضورى

اونلاين

محصل الطالب علي

مقاطع فيديو هات لشرح المقرر بشكل وافي

ملخص للمادة Pdf للمذكرة واطراجة

محاضرات مباشرة علي برنامج زووم

مناقشة الأجزاء الغير مفهومة

تواصل مستمر مع معلم المادة

للتواصل

0567630097



0565657741



Tristates

- Tristate inverter produces Z when not enabled


EN	A	Y
0	0	Z
0	1	Z
1	0	1
1	1	0

  

Multiplexers

- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

 


$$S=0 \quad Y=D_0$$

$$S=1 \quad Y=D_1$$

- Nonrestoring mux uses two transmission gates
 - Only 4 transistors


$$S=0$$

$$S=1$$

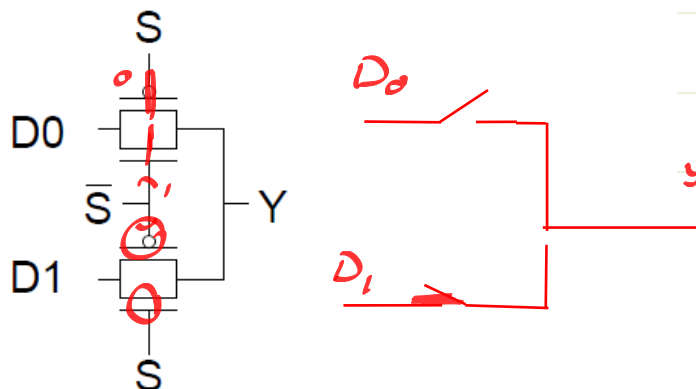

4:1 Multiplexer

 
- 4:1 mux chooses one of 4 inputs using two selects
 - Two levels of 2:1 muxes



S_0	S_1	
0	0	$D_0 = y$
0	1	$D_1 = y$
1	0	$D_2 = y$
1	1	$D_3 = y$





D Latch

 - ❑ When $CLK = 1$, latch is *transparent*
 - D flows through to Q like a buffer
- ❑ When $CLK = 0$, the latch is *opaque*
 - Q holds its old value independent of D
- ❑ a.k.a. *transparent latch* or




- ❑ Multiplexer chooses D or old Q

2:1

  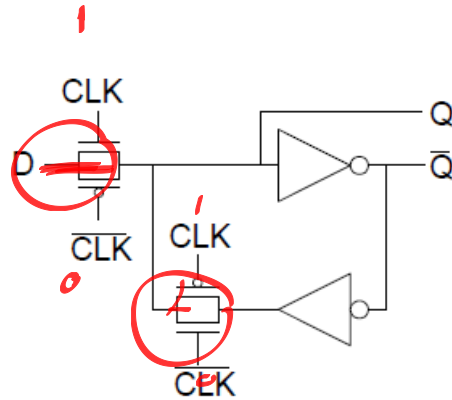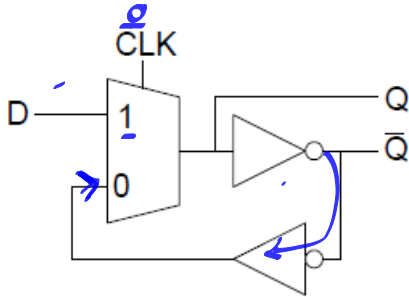

D Flip-flop

 - When CLK rises, D is copied to Q
- At all other times, Q holds its value
- a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*



- Built from master and slave D latches

