

M R
Ahmed Mahdy



فيزياء	استاتيكا
دوائر كهربية	الكثرونيات
ميكانيكا الانشآت	هيدروليكا

مدرس خصوصي

حضورى

اونلاين

بحصل الطالب علي

مقاطع فيديو هات لشرح المقرر بشكل وافى

ملخص للمادة Pdf للمذكرة والمراجعة

محاضرات مباشرة علي برنامج زووم

مناقشة الأجزاء الغير مفهومة

تواصل مستمر مع معلم المادة





للتواصل


0567630097

0565657741

Ohm's Law

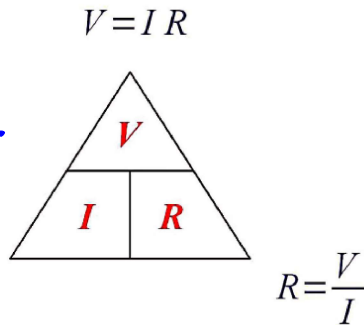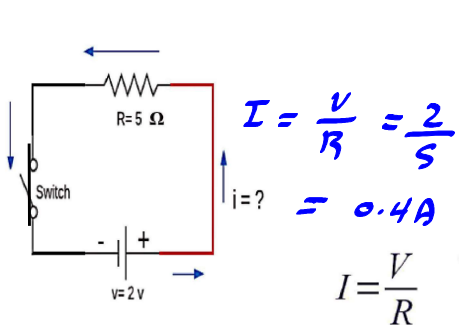

Power

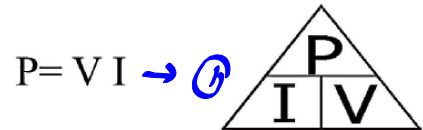


$P = IR I = I^2 R \rightarrow \textcircled{2}$

$P = V \cdot \frac{V}{R} = \frac{V^2}{R} \rightarrow \textcircled{3}$

$\sqrt{\frac{P}{R}} = \sqrt{I^2} = I$




Power and Ohm's Laws

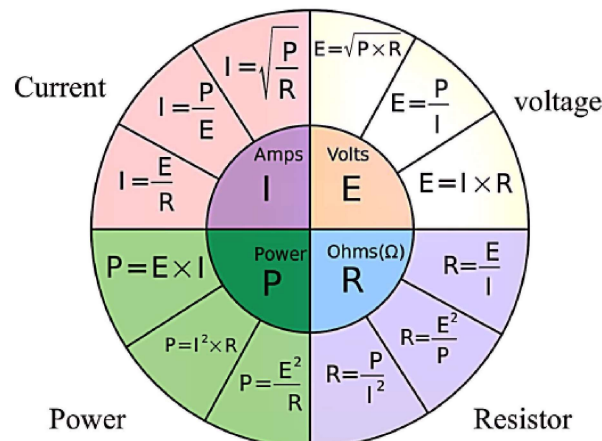

Sign Convention

Voltage:

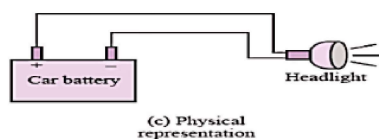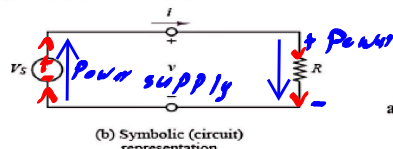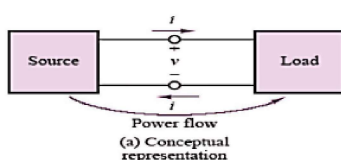
By convention the direction of **positive current** flow out of a voltage source is *out of the positive terminal*.



Positive versus negative current




Positive versus negative voltage

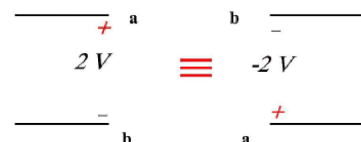


Electric Power and sign Convention

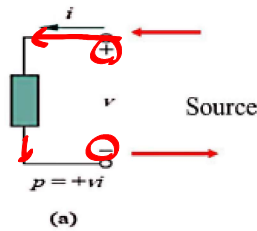Passive sign convention is satisfied when the current enters through the positive terminal of an element and $p = +vi$. If the current enters through the negative terminal, $p = -vi$.





(a) absorbing power,

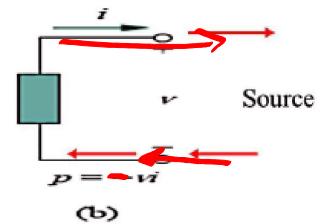


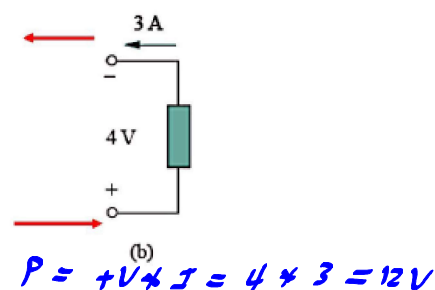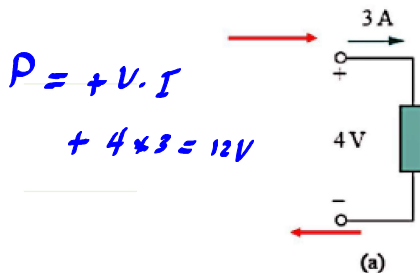(b) supplying power.


- For example, the element in both circuits of Fig. a and b has an absorbing power of +12 W because a positive current enters through the positive terminal in both cases.



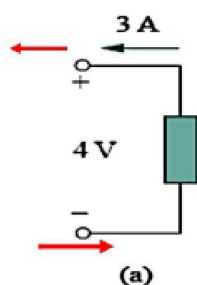- In Fig. a and b the element is supplying power of -12W because a positive current enters through the negative terminal.



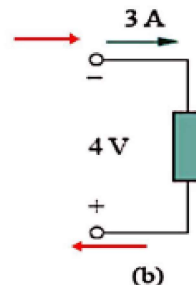$P = -v \cdot I = -4 \times 3 = -12 \text{ W}$



$P = -4 \times 3 = -12 \text{ W}$

قانون حفظ الطاقة


law of conservation of energy

- The law of conservation of energy must be obeyed in any electric circuit. For this reason, the algebraic sum of power in a circuit, at any instant of time, must be zero:


$$\sum P = 0$$

- In other words, in any electric circuit, the total power supplied equals the total power dissipated:
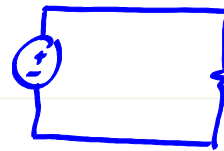
$$\sum P_{\text{sup}} = \sum P_{\text{dis}}$$



Example

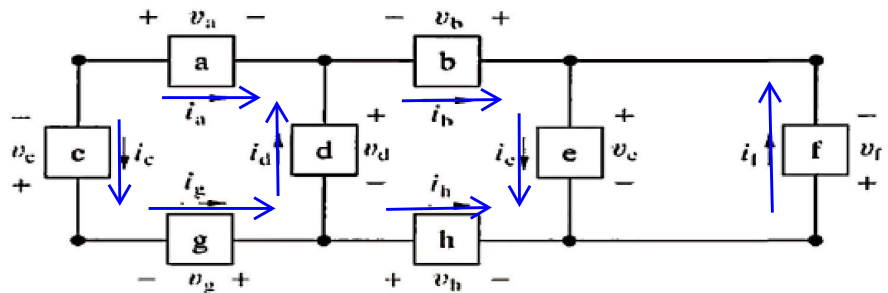

Element	Voltage (V)	Current (mA)	Elements	Type of Elements	Calculation	Supply or Absorbs Power
a	5	2	a	passive	$P_a = v_a i_a = (5)(2\text{m})$	+10 mW (absorbs)
b	1	3	b	active	$P_b = v_b i_b = -(1)(3\text{m})$	-3 mW (supply)
c	7	-2	c	active	$P_c = -7 \times (-2)$	14 mW absorbs
d	-9	1	d	active	$P_d = -(-9)(1)$	9 mW absorbs
e	-20	5	e	passive	$P_e = -20 \times 5$	-100 mW supply
f	20	2	f	passive	$P_f = 20 \times 2$	40 mW absorbs
g	-3	-2	g	active	$P_g = -(-3)(-2)$	-6 mW supply
h	-12	-3	h	passive	$P_h = (-12)(-3)$	36 mW absorbs

$$P_{\text{supply}} = 109 \text{ mW}, \quad P_{\text{dis}} = 109 \text{ mW}$$