

Chapter 1

- 1-1 Determine the current I in the circuit of Figure P1-1.

apply ohm's law

$$I = \frac{V}{R} = \frac{36}{20 \times 10^3} = 1.8 \times 10^{-3} \text{ A} = 1.8 \text{ mA}$$

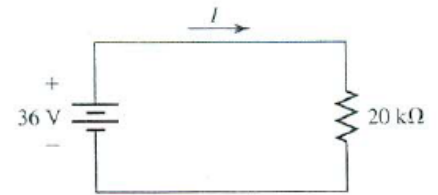


FIGURE P1-1

- 1-2 Determine the current I in the circuit of Figure P1-2.

apply ohm's law

$$I = \frac{V}{R} = \frac{80}{16} = 5 \text{ A}$$

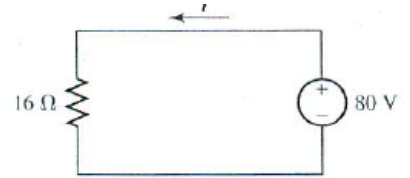


FIGURE P1-2

- 1-3 Determine the current I in the circuit of Figure P1-3.

$$I = \frac{V}{R} = \frac{-6}{2 \times 10^3} = -3 \times 10^{-3} \text{ A} = -3 \text{ mA}$$

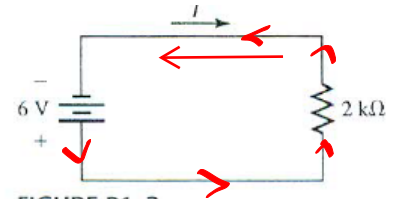


FIGURE P1-3

- 1-4 Determine the current I in the circuit of Figure P1-4.

$$I = \frac{V}{R} = \frac{30}{1 \times 10^6} = 30 \times 10^{-6} \text{ A} = 30 \text{ } \mu\text{A}$$

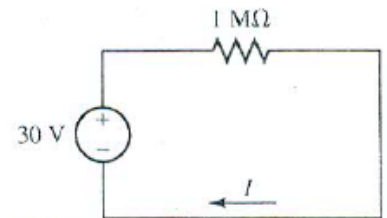


FIGURE P1-4

- 1-5 Determine the power delivered by the source in Problem 1-1.

$P = I \cdot V = \frac{V^2}{R} = I^2 R$

$$P = \frac{V^2}{R} = \frac{(36)^2}{20 \times 10^3} = 64.8 \times 10^{-3} \text{ W} = 64.8 \text{ mW}$$

- 1-6 Determine the power delivered by the source in Problem 1-2.

$$P = \frac{V^2}{R} = \frac{(80)^2}{16} = 400 \text{ W}$$

- 1-7 Determine the power delivered by the source in Problem 1-3.

$$P = \frac{V^2}{R} = \frac{(6)^2}{2 \times 10^3} = 18 \times 10^{-3} \text{ W} = 18 \text{ mW}$$

- 1-8 Determine the power delivered by the source in Problem 1-4.

$$P = \frac{V^2}{R} = \frac{(30)^2}{1 \times 10^6} = 900 \times 10^{-6} \text{ W} = 0.9 \text{ mW}$$

- 1-9 Determine the voltage V in the circuit of Figure P1-9.

apply ohm's law

$$V = RI = 3 \times 10^3 \times 2 \times 10^{-3} = 6 \text{ V}$$

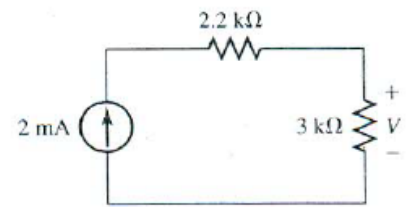


FIGURE P1-9

- 1-10 Determine the voltage V in the circuit of Figure P1-10.

$$V = RI = 3 \times 10^3 \times (-2 \times 10^{-3}) = -6 \text{ V}$$

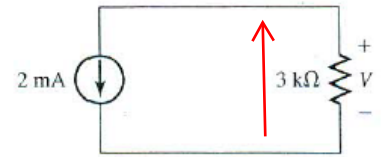


FIGURE P1-10 *V = -6V*

- 1-11 Determine the resistance of a 20-W bulb operating from a dc voltage of 12 V.

P = 20 W

$$P = I^2 R = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P}$$

$$\text{Since } P = \frac{V^2}{R}, \text{ then } R = \frac{V^2}{P} = \frac{(12)^2}{20} = 7.2 \Omega$$

- 1-12 Determine the resistance of a 500-W heating element operating from an ac effective voltage of 120 V. *V = 120 V*

P = 500 W

$$\text{Since } P = \frac{V^2}{R}, \text{ then } R = \frac{V^2}{P} = \frac{(120)^2}{500} = 28.8 \Omega$$

I??, V??

$$P = 1000 \text{ W}, R = 50 \Omega$$

- 1-13 A radio transmitter has an ac average power input of 1 kW with no modulation and it acts effectively as a resistance of value 50 Ω. Determine the ac effective current and the ac effective voltage.

$$\text{Since } P = I^2 R, \text{ then } I = \sqrt{\frac{P}{R}} = \sqrt{\frac{1000}{50}} = 4.472 \text{ A},$$

$$\text{Since } P = \frac{V^2}{R}, \text{ then } V = \sqrt{RP} = \sqrt{50 \times 1000} = 223.6 \text{ V}$$

$$\text{Check: } R = \frac{V}{I} = \frac{223.6}{4.472} = 50 \Omega$$

V = IR = 4.472 \times 50

R = 50 \Omega

- 1-14 The power dissipated in a certain resistance of 20 Ω is 500 W. Determine the current and the voltage.

P = 500 W

$$\text{Since } P = I^2 R, \text{ then } I = \sqrt{\frac{P}{R}} = \sqrt{\frac{500}{20}} = 5 \text{ A}$$

$$\text{Since } P = \frac{V^2}{R}, \text{ then } V = \sqrt{RP} = \sqrt{20 \times 500} = 100 \text{ V}$$

$$\text{Check: } R = \frac{V}{I} = \frac{100}{5} = 20 \Omega$$

$$V_{AB} =$$

$$A = 40 \text{ V}$$

$$B = 22 \text{ V}$$

- 1-15 Various voltages in a circuit are measured with respect to a common ground reference. The voltage at point A is 40 V and the voltage at point B is 22 V. Determine the voltage V_{AB} .

$$V_{AB} = V_A - V_B = 40 - 22 = 18 \text{ V}$$

- 1-16 Repeat the analysis of Problem 1-15 if the voltage at point A is 12 V and the voltage at point B is -20 V.

$$V_{AB} = V_A - V_B = 12 - (-20) = 12 + 20 = 32 \text{ V}$$

- 1-17 The voltage across a resistance is 15 V and the current is 0.5 mA. Determine the resistance.

$$R = \frac{V}{I} = \frac{15}{0.5 \times 10^{-3}} = 30 \times 10^3 \Omega = 30 \text{ k}\Omega$$

- 1-18 The voltage across a resistance is 10 V and the current is $2 \mu\text{A}$. Determine the resistance.

$$R = \frac{V}{I} = \frac{10}{2 \times 10^{-6}} = 5 \times 10^6 \Omega = 5 \text{ M}\Omega$$

$$E = P t$$

$$\text{Cost} = E \cdot C$$

- 1-19 Determine the cost of leaving a 10-W bulb on for one year if electricity costs \$0.09 per kilowatt-hour. (Assume that it is not a leap year!)

$$W(\text{W.hr}) = (10 \text{ W}) \times (365 \text{ days}) \times (24 \text{ hours/day}) \times (1/1000) \text{ kW/W} = 87.6 \text{ kW.hr}$$

$$\text{Cost} = (87.6 \text{ kW.hr}) \times (0.09 / \text{kW.hr}) = \$7.88$$

$$P = 10 \times 10^{-3} \text{ kW}$$

$$t = 365 \times 24 \text{ h}$$

$$C = 0.09 \$$$

- 1-20 Determine the energy in joules dissipated in the bulb of Problem 1-19 in one year.

$$P = 10 \text{ W}, t = 365 \times 24 \times 60 \times 60$$

$$W = (10 \text{ W}) \times (3600 \text{ s/hour}) \times (24 \text{ hours/day}) \times (365 \text{ days/year})$$

$$= 315.36 \times 10^6 \text{ J} = 315.36 \text{ MJ}$$

- 1-21 Determine the voltages V_1 and V_2 in Figure P1-21.

$$24 - 6 - 8 - V_1 = 0, V_1 = 10 \text{ V}$$

$$32 + 24 - 6 - 8 + V_2 = 0, V_2 = -42 \text{ V}$$

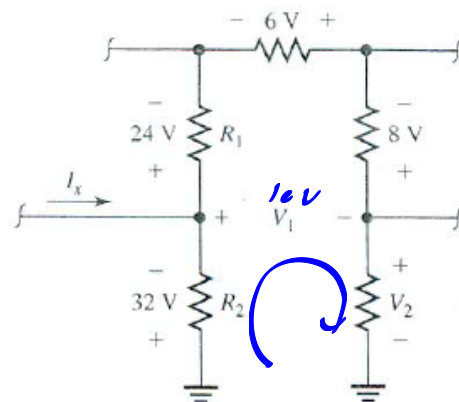


FIGURE P1-21

- 1-22 Determine the voltage V_x in Figure P1-22.

$$32 - 18 + 20 - 60 + V_x = 0, V_x = 26 \text{ V}$$

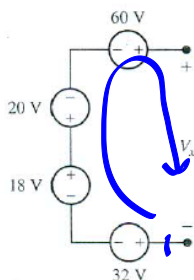


FIGURE P1-22