

M R
Ahmed Mahdy



فيزياء	استاتيكا
دوائر كهربية	الكثرونيات
ميكانيكا الانشآت	هيدروليكا

مدرس خصوصي

حضورى

اونلاين

بحصل الطالب علي

مقاطع فيديو هات لشرح المقرر بشكل وافى

ملخص للمادة Pdf للمذكرة والمراجعة

محاضرات مباشرة علي برنامج زووم

مناقشة الأجزاء الغير مفهومة

تواصل مستمر مع معلم المادة



للتواصل

0567630097

0565657741

Lecture Contents


$$V = IR$$

- Ohm's Law.
- Independent and Dependent Sources.
- Circuit Terminology.
- Kirchhoff's Current Law (KCL).
- Kirchhoff's Voltage Law (KVL).
- Short and Open Circuit.

Ohm's Law

- **Ohm's law** states that the voltage across a resistor is V directly proportional to the current I flowing through the resistor.
- Mathematical expression for Ohm's Law is as follows:

$$v = iR$$

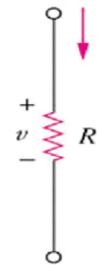

Materials in general have a characteristic behavior of resisting the flow of electric charge. This physical property, or ability to resist current, is known as **Resistance** and is represented by the symbol R .

- **Conductance** G S is the ability of an element to conduct electric current; it is the reciprocal of resistance R and is measured in mhos or siemens.

- The power dissipated by a resistor:

$$G = \frac{1}{R} = \frac{i}{v}$$

$$p = vi = i^2 R = \frac{v^2}{R}$$


Example

- In the circuit shown in Fig. calculate the current i , the conductance G , and the power P .

$$I = \frac{V}{R} = \frac{30V}{5 \times 10^3 \Omega} = 6 \times 10^{-3} A = 6 mA$$

$$G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \times 10^{-3} S = 0.2 mS$$
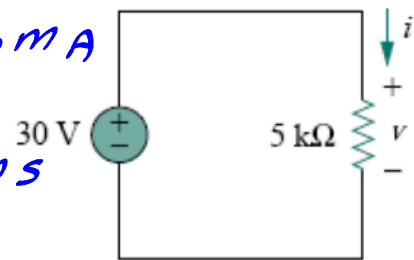
$$P = I \cdot V = 6 \times 10^{-3} \times 30 = 0.18 W = 180 mW$$




Ohms Law

- The **resistance** of any material with a uniform cross-sectional area A depends on A , its length L , and resistivity of the material ρ .
- In mathematical form

$$R = \rho \frac{\ell}{A}$$

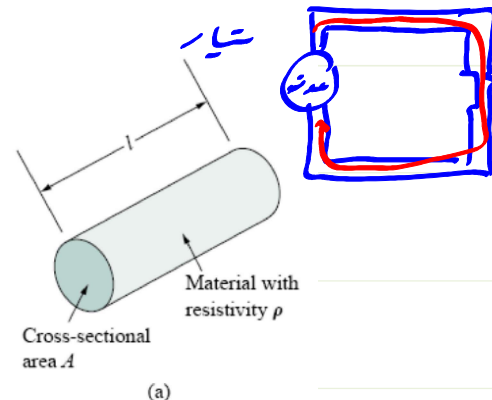where ρ is known as the *resistivity* of the material in ohm-meters.



Resistivity of common materials

The next table presents the values of ρ for some common materials and shows which materials are used for conductors, insulators, and semiconductors.


TABLE 2.1 Resistivities of common materials.

Material	Resistivity ($\Omega \cdot m$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Aluminum	2.8×10^{-8}	Conductor
Gold	2.45×10^{-8}	Conductor
Carbon	4×10^{-5}	Semiconductor

TABLE 2.1 Resistivities of common materials.

Material	Resistivity ($\Omega \cdot m$)	Usage
Germanium	47×10^{-2}	Semiconductor
Silicon	6.4×10^2	Semiconductor
Paper	10^{10}	Insulator
Mica	5×10^{11}	Insulator
Glass	10^{12}	Insulator
Teflon	3×10^{12}	Insulator

Ohm's Law Conclusion

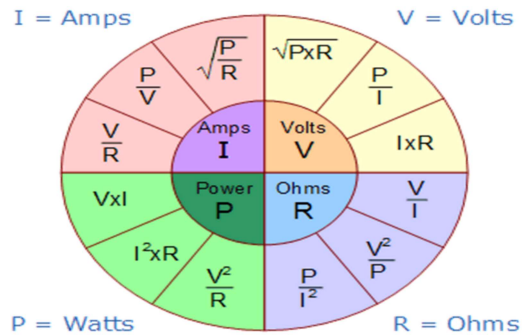

Independent vs. Dependent Sources




There are two kinds of sources:

1. An **independent source** (voltage or current) may be DC (constant) or time-varying, but does not depend on other voltages or currents in the circuit.
2. A **dependent source's** value depends on another voltage or current in the circuit.

SOURCES


independent

dependent

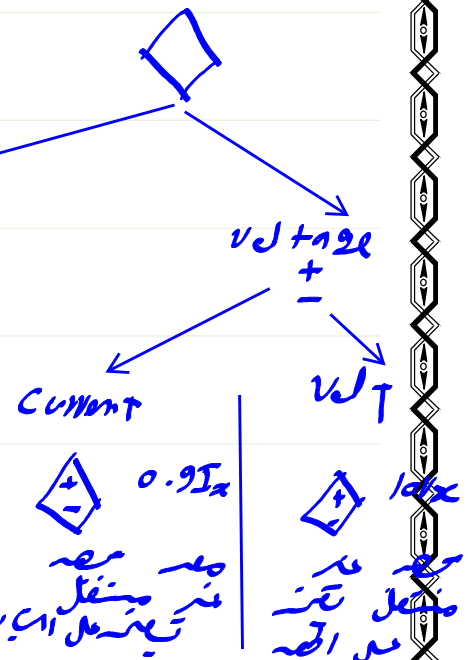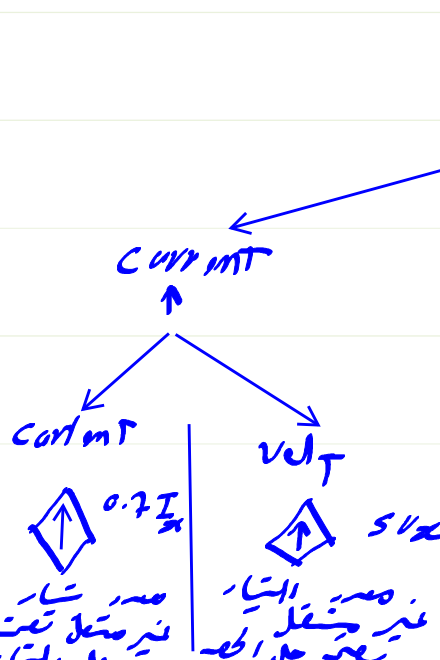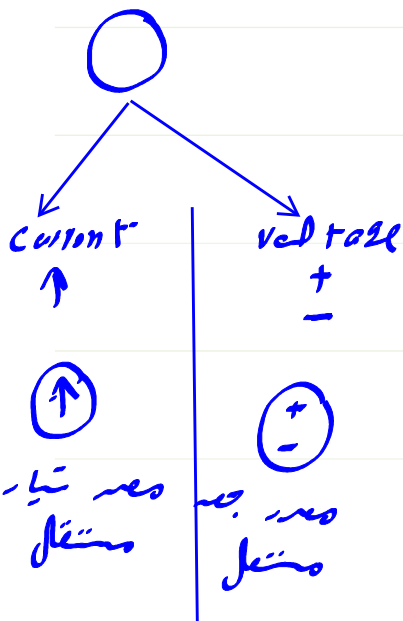

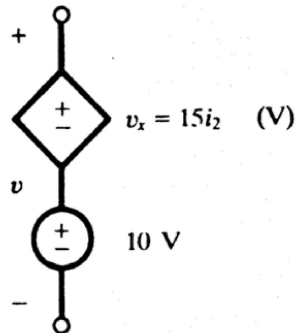Example 2


Obtain the voltage v in the branch shown in the Figure for $i_2 = 1\text{A}$.



$$V = 15 \times 1 + 10 = 25\text{V}$$


Circuit Terminology

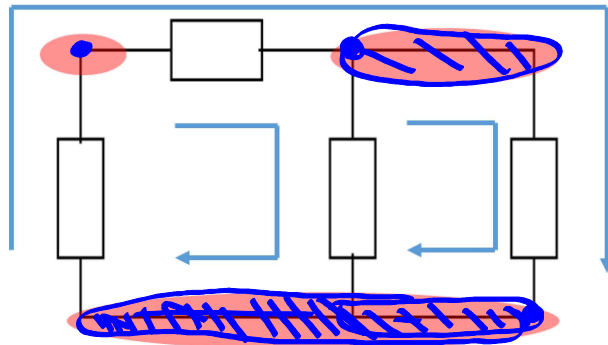- **Node:** A point where two or more elements join.
- **Loop:** Any closed path in a circuit.
- **Mesh:** A loop not containing other loops.



3 Node.
 3 Loop.
 2 Mesh.

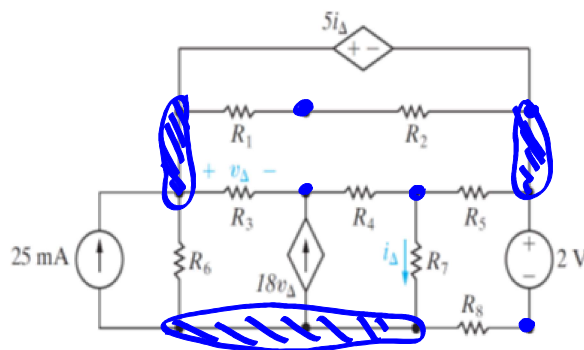Example: for the circuit shown in Figure, find the number of nodes, meshes, and loops:




7 nodes
 6 mesh
 7 loops

استی-الکد؟ = ایت، ابراهیل
 $i_1 + i_3 + i_4 = i_2 + i_5$

Kirchhoff's Current Law (KCL)

Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node is zero.


نیا-الکد؟ تیر-ابراهیل
 $-$ $+$

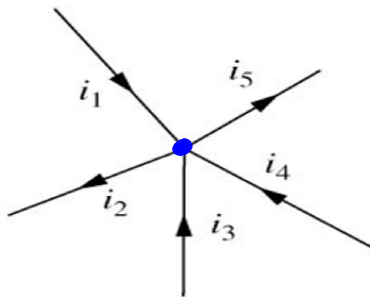

$$\sum_{n=1}^N i_n = 0$$

$$-i_1 + i_2 - i_3 - i_4 + i_5 = 0$$

Example for KCL

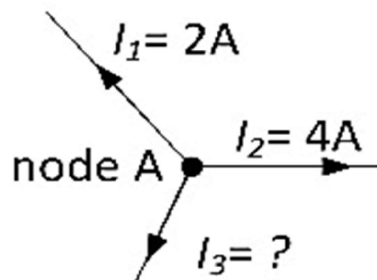


$$i_3 + i_2 + i_1 = 0$$

$$i_3 + 4 + 2 = 0$$

$$i_3 = -6A$$

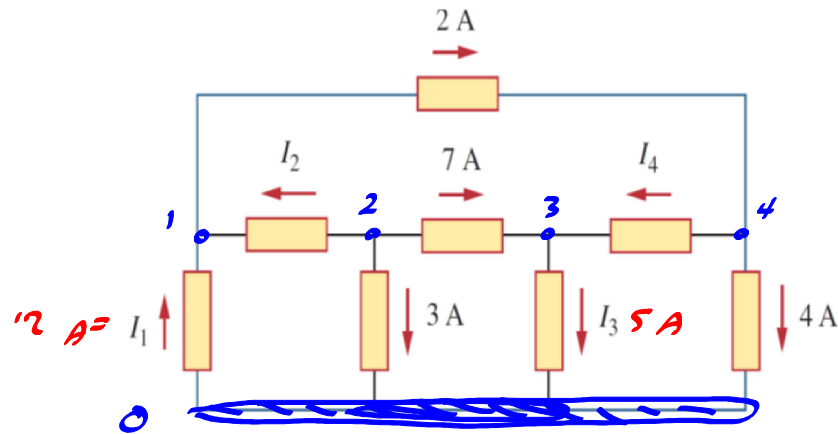Example1: For the circuit, use KCL to find the branch currents I_1 to I_4 :



apply K.C.l at node 1

$$-I_1 - I_2 + 2 = 0 \Rightarrow -I_1 - (-10) + 2 = 0 \Rightarrow I_1 = 12A$$

apply K.C.l at node 2

$$I_2 + 3 + 7 = 0 \Rightarrow I_2 = -10A$$

apply K.C.l at node 4

$$-2 + I_4 + 4 = 0 \Rightarrow I_4 = -2A$$


apply K.C.l at node 3

$$-7 + I_3 - (-2) = 0 \Rightarrow I_3 = 5A$$

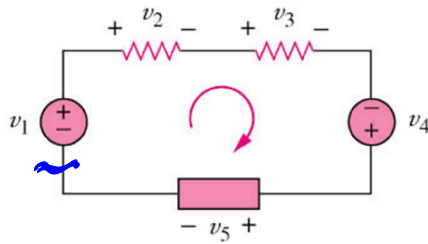15. v. l

KIRCHHOFF VOLTAGE LAW

Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.




Mathematically,

$$\sum_{n=1}^M v_n = 0$$

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

Ex. write the KVL for the circuit shown

$$v_4 - v_3 - v_3 + v_1 - v_5 = 0$$

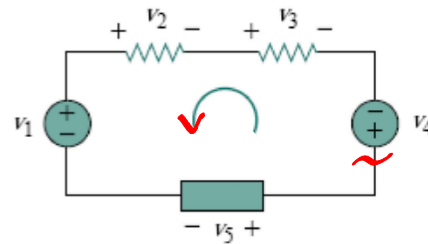

$$V = IR$$


Example 1

If $V_o = -6i_o$, determine i and V_o in the circuit shown in Fig.

apply K.V.L

$$-12 + V_1 + 2V_o - 4 + V_2 = 0$$

$$-2L = 16$$

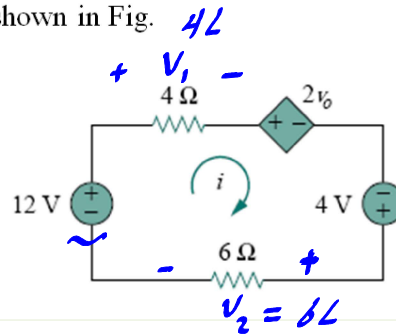

$$L = -8A$$

$$V_o = -6(-8) = 48V$$

Example 2


Find current I and voltage V in the circuit shown in Fig.

apply K.C.L at a

$$-0.5I_o + I_o - 3 = 0$$

$$0.5I_o = 3 \Rightarrow I_o = 6A$$


$$V_o = 6 \times 4 = 24V$$

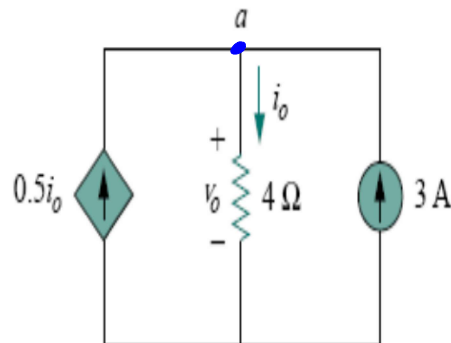

$$V = IR, \text{ K.C.L, K.V.L}$$

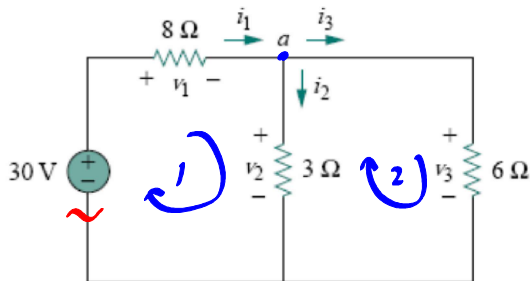Example 3

Find the currents and voltages in the circuit shown in Fig. (a).



(a)

apply K.C.L at node a

$$-I_1 + I_2 + I_3 = 0 \rightarrow \textcircled{1}$$

apply K.V.L at mesh 1

$$-30 + \overset{8I_1}{V_1} + \overset{3I_2}{V_2} = 0$$

$$8I_1 + 3I_2 = 30 \rightarrow \textcircled{2}$$

apply K.V.L at mesh 2

$$-\overset{3I_2}{V_2} + \overset{6I_3}{V_3} = 0$$

$$-3I_2 + 6I_3 = 0 \rightarrow \textcircled{3}$$

$$V_1 = 24V, \quad V_2 = 6V, \quad V_3 = 6V$$

$$-I_1 + I_2 + I_3 = 0$$

$$8I_1 + 3I_2 = 30$$

$$-3I_2 + 6I_3 = 0$$

$$I_1 = 3A, \quad I_2 = 2A, \quad I_3 = 1A$$