



مدرس خصوصى




اونلاين

يحصل الطالب على ...

- * مقاطع فيديو هات لشرح المقرر بشكل وافي
- * ملخص للمادة للمراجعة النهائية
- * محاضرات مباشرة على برنامج Zoom
- * تواصل مستمر مع معلم المادة للمناقشة



للتواصل

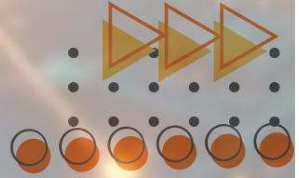

00201024041097



00201096019763

Mrahmedmahdy.com



ELECTRICAL CIRCUITS

SYSTEMS OF UNIT

Table 1.2 SI units

Quantity	Unit	Symbol
Length	Meter	m
Mass	Kilogram	kg
Time	Second	s
Electric current	Ampere	A
Temperature	Kelvin	K
Luminous intensity	Candela	cd

Table 1.3 Standard prefixes

Prefix	Symbol	Power
atto	a	10^{-18}
femto	f	10^{-15}
pico	p	10^{-12}
nano	n	10^{-9}
micro	μ	10^{-6}
milli	m	10^{-3}
centi	c	10^{-2}
deci	d	10^{-1}
deka	da	10
kilo	k	10^3
mega	M	10^6
giga	G	10^9
tera	T	10^{12}

$$V = \frac{J}{C} = \frac{m}{s}$$

$$3000\text{ m} = 3\text{ km}$$




$$3000000\text{ m} = 3\text{ Mm}$$

$$0.02\text{ m} = 2\text{ cm}$$


$$0.002\text{ m} = 0.2\text{ cm} = 2\text{ mm}$$

SOURCE-LOAD REPRESENTATION

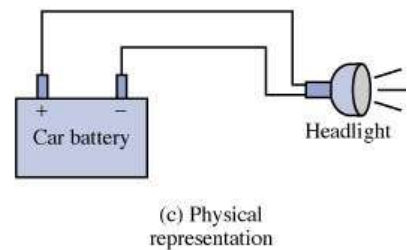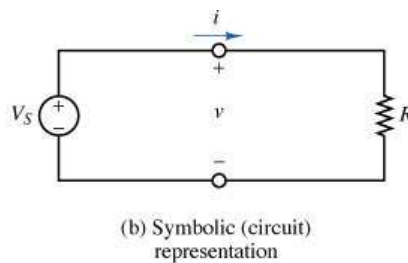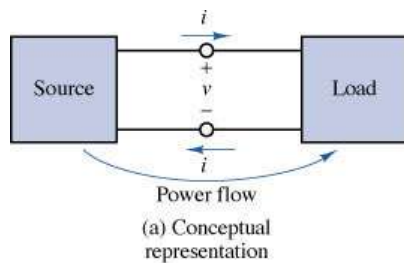
$$\frac{I}{A} = \frac{V}{V} = \frac{R}{\Omega} = \frac{P}{W}$$



Ideal voltage Source

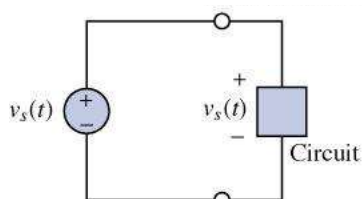


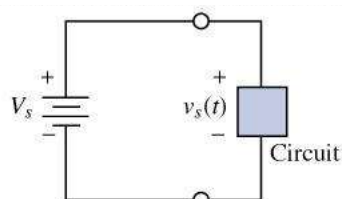General symbol for ideal voltage source. $v_s(t)$ may be constant (DC source).




A special case: DC voltage source (ideal battery)

Ideal Current Source

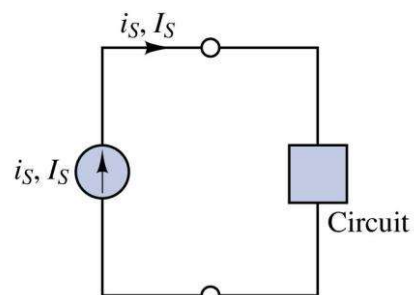


DEFINITION OF A BRANCH

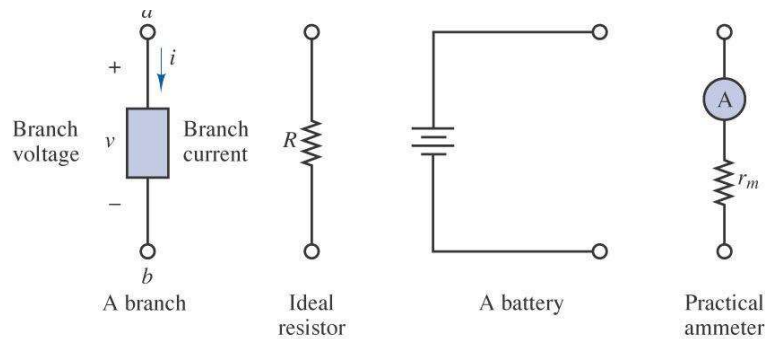


Examples of circuit branches

Definition of node and super node

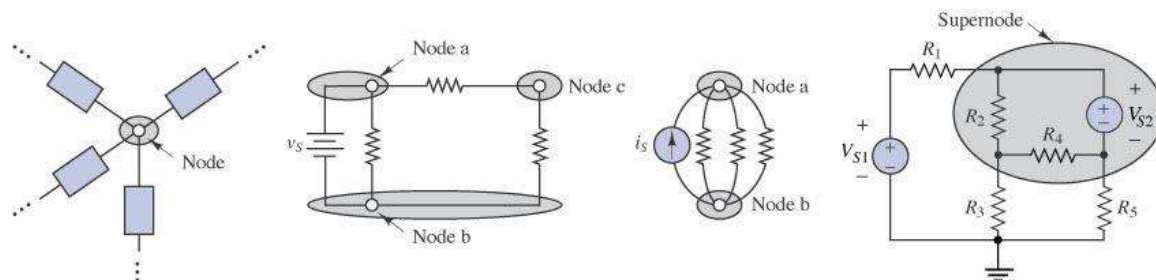


DEFINITION OF LOOP

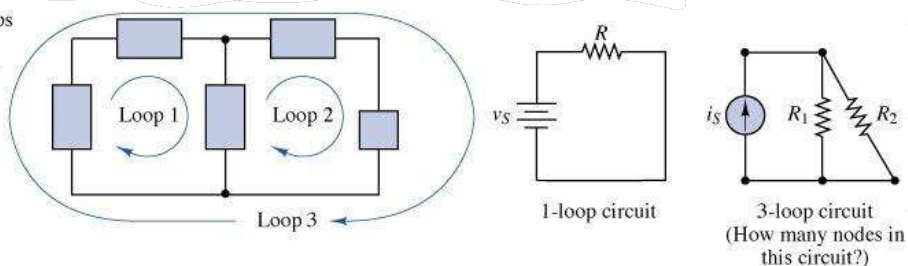Note how two different loops in the same circuit may include some of the same elements or branches.




Definition of Mesh

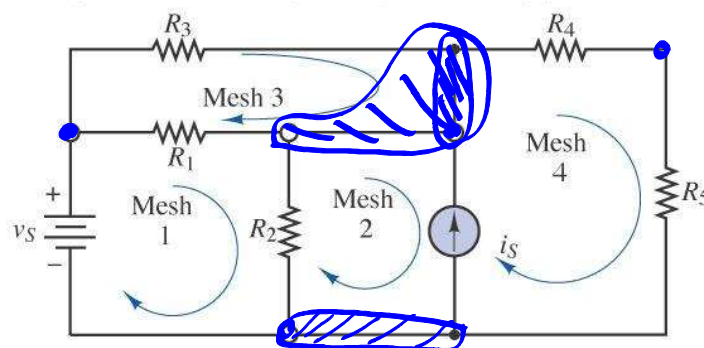How many loops can you identify in this four-mesh circuit? (Answer: 15)





CHARGE, CURRENT & KCL

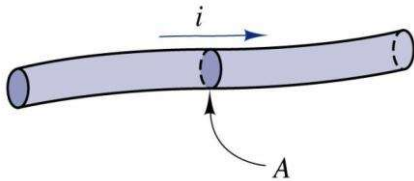Current $i = dq/dt$ is generated by the flow of charge through the cross-sectional area A in a conductor.



Kirchhoff's Current Law (KCL):

مجموع التيارات = صفر في العقد
K.C.L

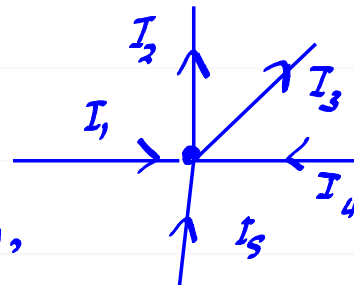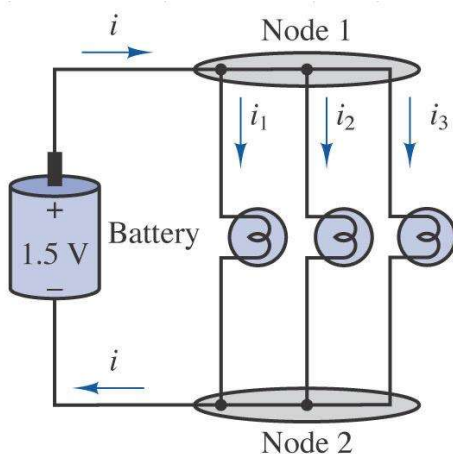

داخل
خارج

$$\sum I_n = 0$$

$$+ I_1 - I_2 - I_3 + I_4 + I_5 = 0$$

$$I - I_1 - I_2 - I_3 = 0$$

EXAMPLE 2.3

Given: $I_s = 5A$, $I_1 = 2A$, $I_2 = -3A$, $I_3 = 1.5A$

Calculate I_0 and I_4

طبق K.C.L at a


$$-I_0 - I_1 - I_2 = 0$$

$$-2 - (-3) = I_0$$

$$I_0 = 1A$$

$$I_s + I_0 + I_1 + I_2 - I_3 - I_4 = 0$$

$$5 + 1 + 2 - 3 - I_4 = 0 \rightarrow I_4 = 3.5A$$

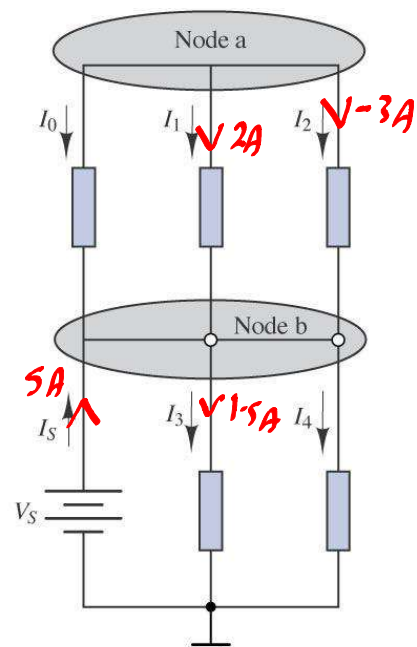

Example 2.4


Given: $I_3=2A$, $I_5=0A$

Find I_{s1}



apply K.C.L at b

$$+ \cancel{I_5} + I_3 - I_{s1} = 0$$

$$I_{s1} = I_3 = 2A$$

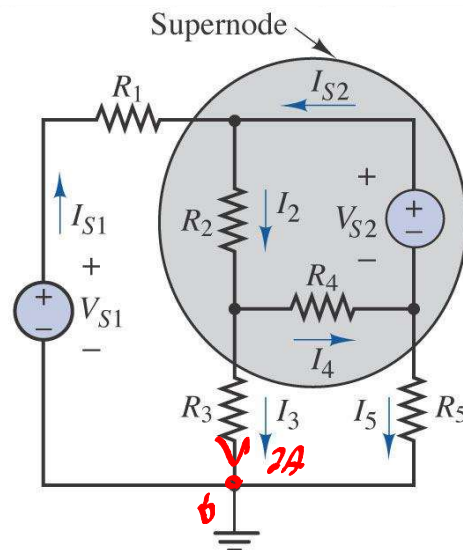

Kirchhoff's Voltage Law (KVL):

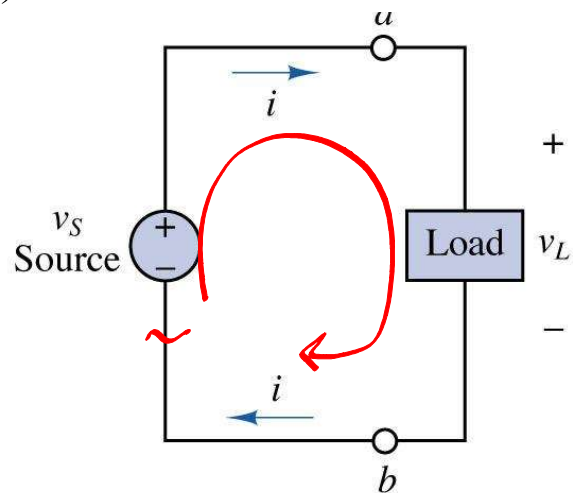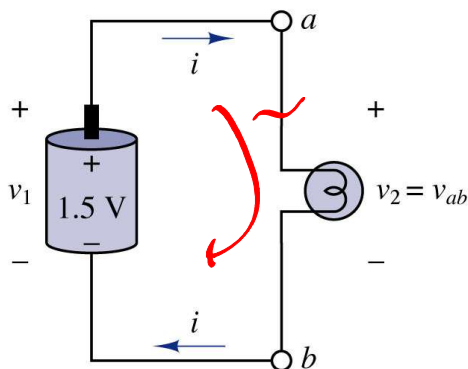

مجموع الجهود على أي مسار مغلق يساوي صفر

$$\sum_{n=1}^N V_n = 0$$

$$-V_1 + V_L = 0$$


$$V_{ab} - 1.5V = 0$$

Example 2.6

Given: $V_{s2}=12V$, $V_1=6V$, $V_3=1V$

Find V_2

apply K.V.L

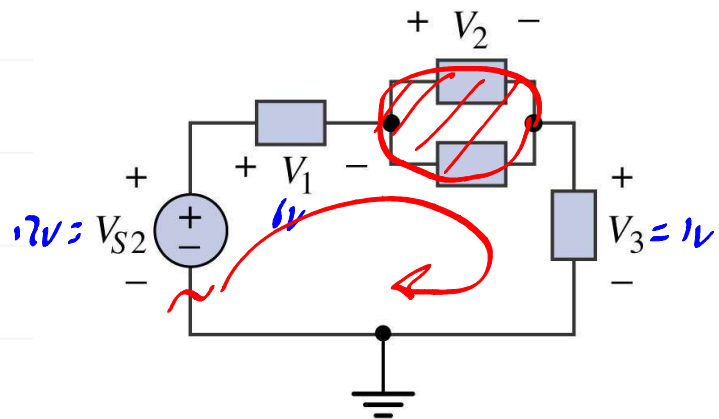

$$-V_{s2} + V_1 + V_2 + V_3 = 0$$

$$-12 + 6 + V_2 + 1 = 0$$

$$V_2 = 5V$$