

Electric Circuits Elements

Lec 02

Contents

- Basic circuit elements : Active element and Passive element

Active and Passive Circuit Elements

A **passive element** absorbs (dissipates) energy.

An **active element** is capable of supplying energy.

ACTIVE ELEMENT AND PASSIVE ELEMENT

Active Element – elements capable of generating electrical energy. For example:

Voltage source

Current source


Passive Element – elements are not capable of generating electrical energy. For example:

Resistor (dissipates energy)


Capacitor and Inductor (can store or release energy)

Independent source

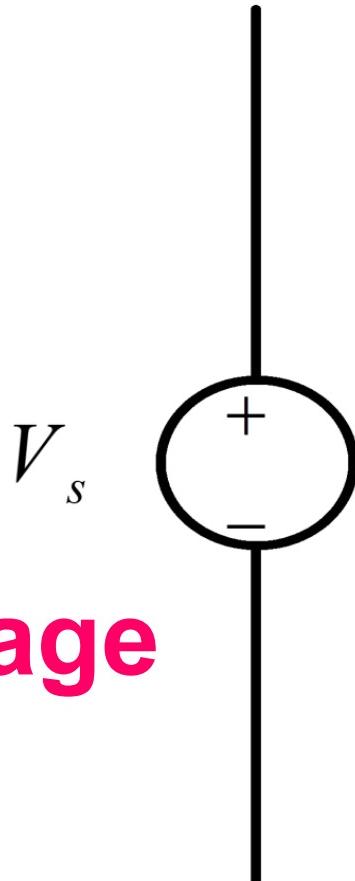This source maintains a specified voltage between its terminals but has no control on the current passing through it. The symbol of the independent voltage source is a plus-minus sign enclosed by a circle.



Voltage

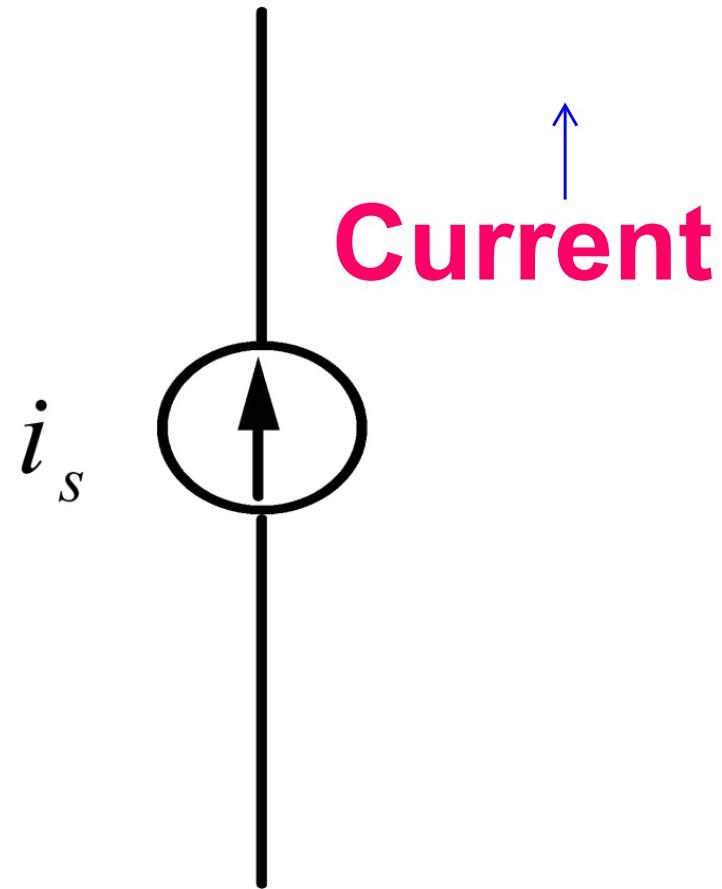


Current


This source maintains a specified current through its terminals but has no control on the voltage across its terminals. The symbol of the independent current source is an arrow enclosed by a circle.

Dependent source

Voltage

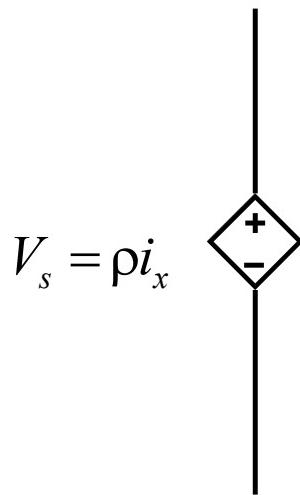

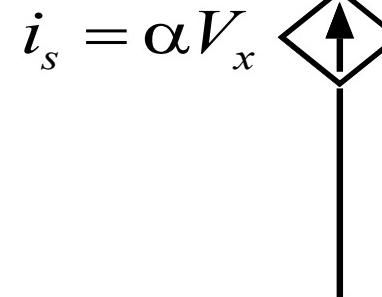
This kind of voltage source has a specified voltage between its terminals but it is dependable on some other variable defined somewhere in the circuit. The symbol for the dependent voltage source is a plus-minus sign enclosed by a diamond shape. The value of the dependent current source is ρi_x (ohms) where ρ is the scale factor or gain.



Current

This kind of current source has a specified current between its terminals but it is dependent on some other variable defined somewhere in the circuit. The symbol for the dependent current source is an arrow enclosed by a diamond shape. The value of the dependent current source is αV_x (in Siemens) where α is the scale factor or gain.


VOLTAGE AND CURRENT SOURCES

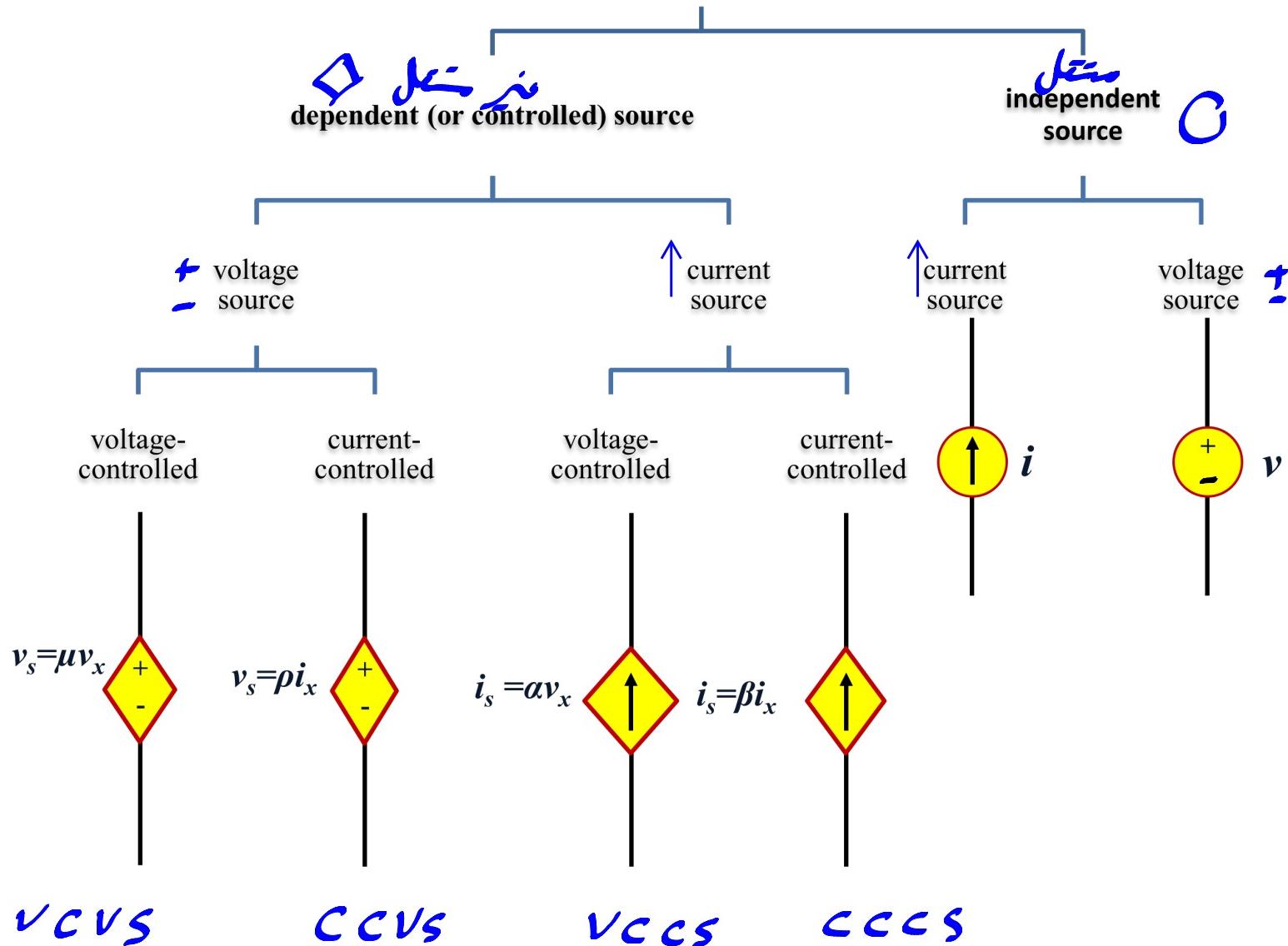

EXAMPLE


obtain the voltage v in the branch shown in figure below for $i_2 = 1\text{A}$.

$$v = 10 + v_x = 10 + 15(1) = 25$$

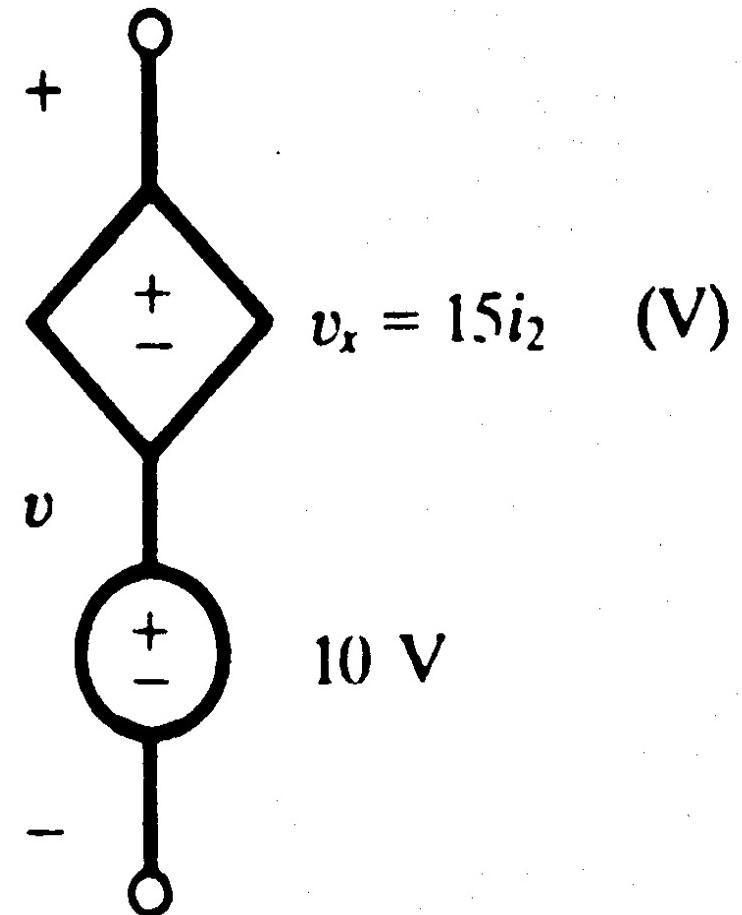

Circuit symbol of resistor

Resistor

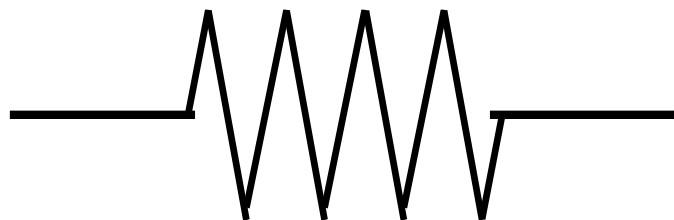


R

Resistor is passive element that dissipates electrical energy. Linear resistor is the resistor that obeys Ohm's law.


UNIT: Ohm (Ω)

RESISTOR COLOUR CODE

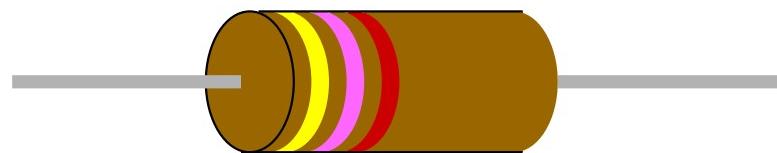



Color	Color Name	1st Digit 1st Stripe	2nd Digit 2nd Stripe	Multiplier 3rd Stripe	Tolerance 4th Stripe
Black	Black	0	0	x1	-
Brown	Brown	1	1	x10	-
Red	Red	2	2	x100	-
Orange	Orange	3	3	x1,000	-
Yellow	Yellow	4	4	x10,000	-
Green	Green	5	5	x100,000	-
Blue	Blue	6	6	x1,000,000	-
Violet	Violet	7	7	-	-
Gray	Gray	8	8	-	-
White	White	9	9	-	-
Gold	Gold	-	-	-	5%
Silver	Silver	-	-	-	10%

Resistor Colour Codes

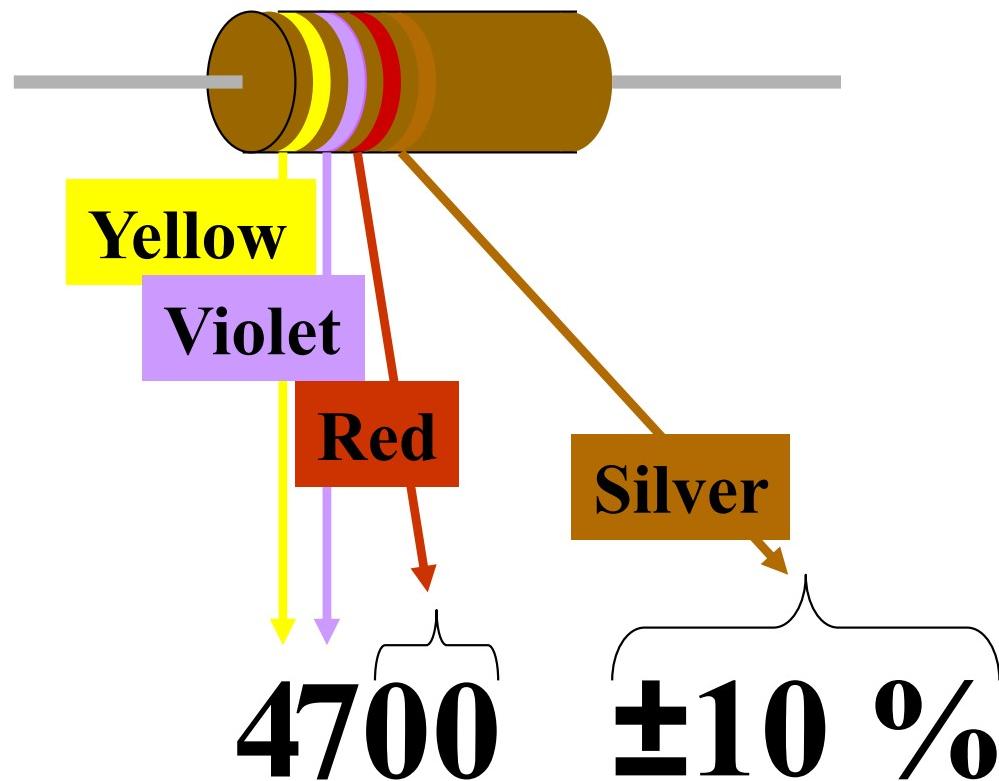

RESISTORS

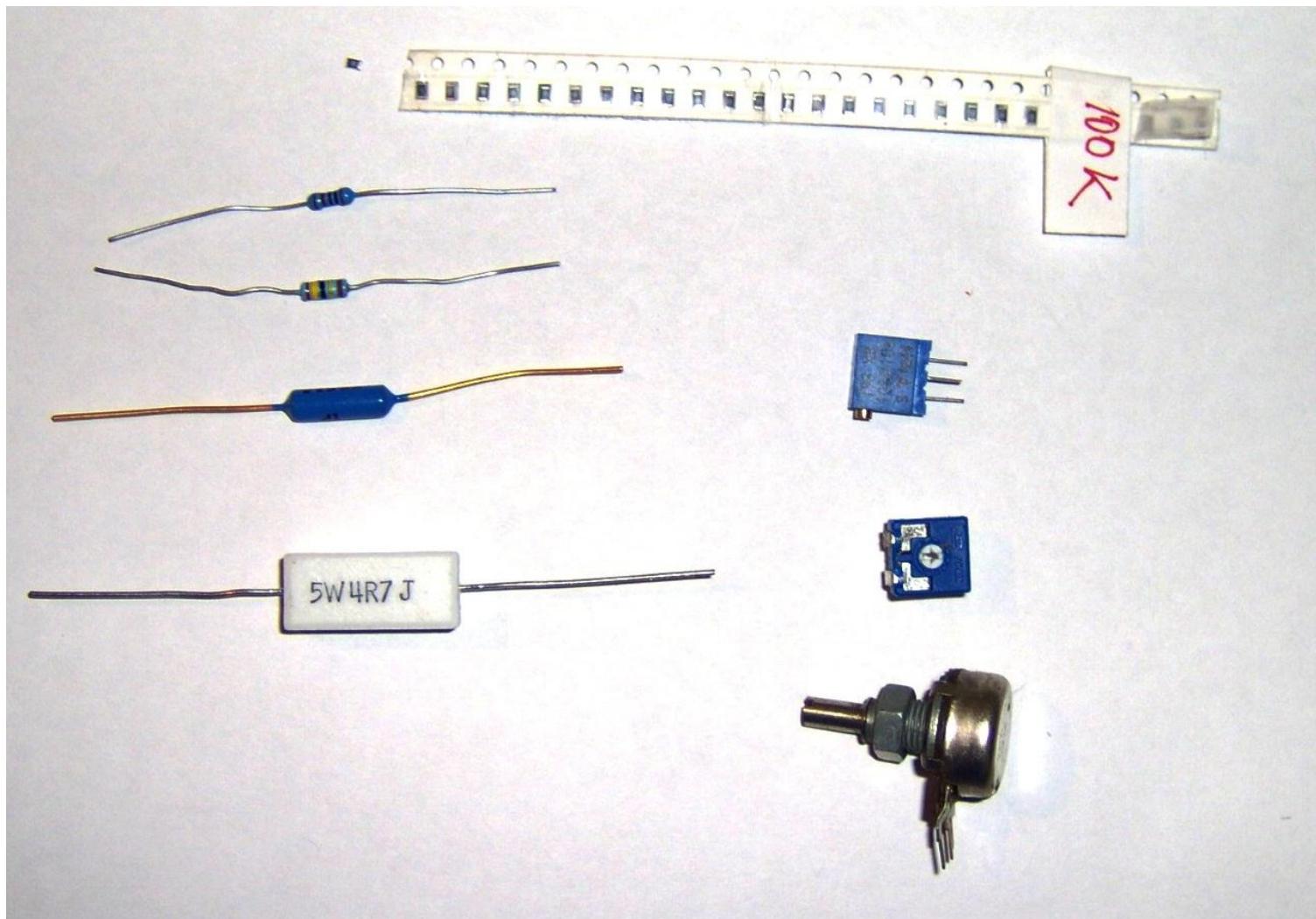

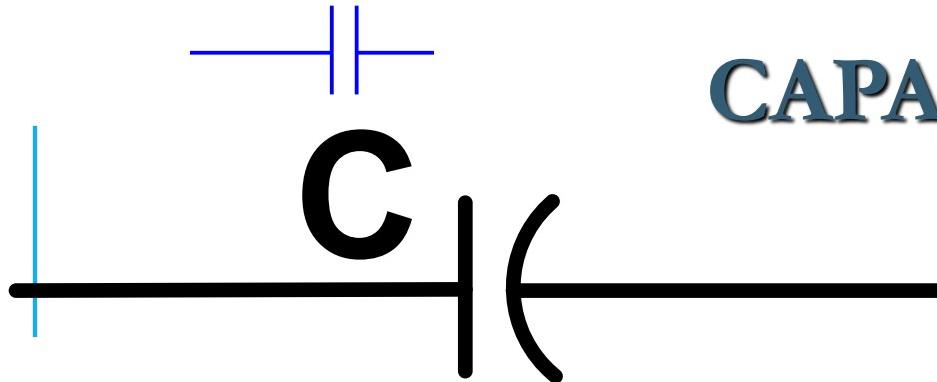

CAPACITOR

UNIT: Farad (F)


Electrical component that consists of two conductors separated by an insulator or dielectric material.

Its behavior based on phenomenon associated with electric fields, which the source is voltage.

A time-varying electric fields produce a current flow in the space occupied by the fields.


Capacitance is the circuit parameter which relates the displacement current to the voltage.

CAPACITORS

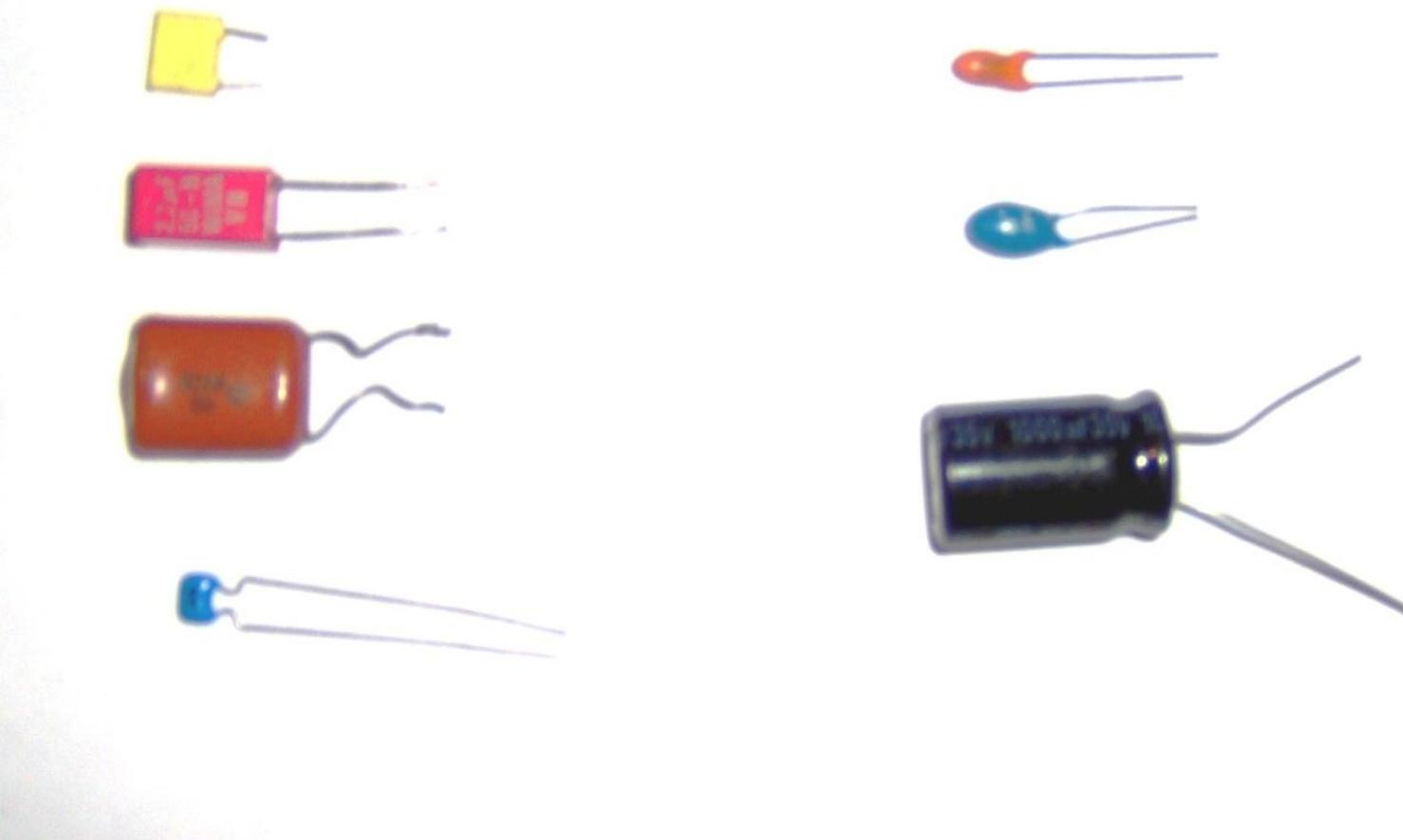


A capacitor with an applied voltage

Conducting plates
each with area A

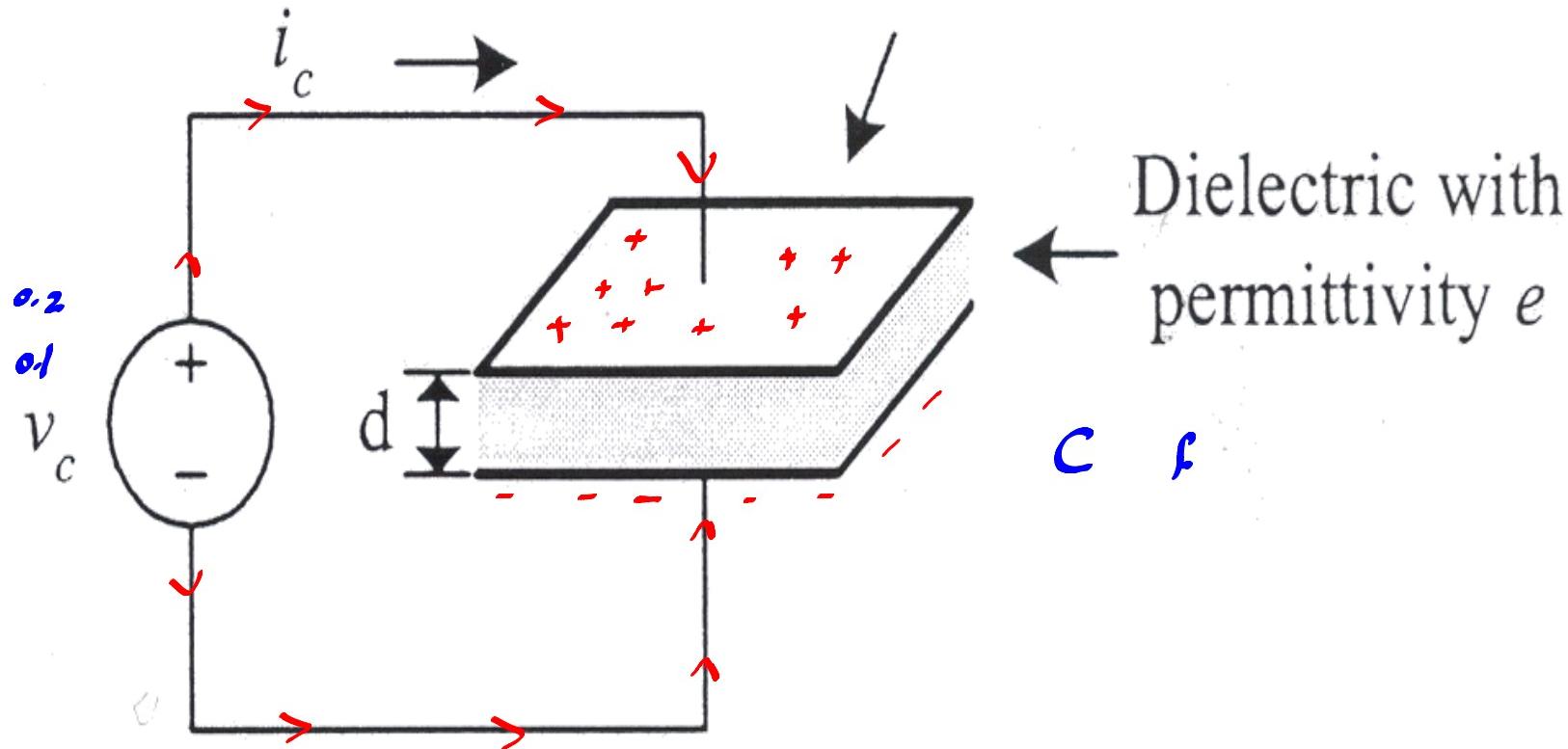

Plates - aluminum foil

Dielectric - air/ceramic/paper/mica

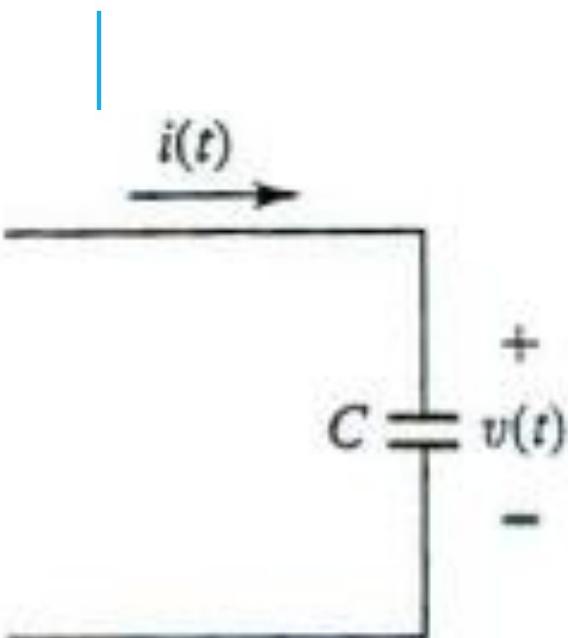

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$

FIGURE 3–3
 Capacitance with instantaneous
 time-varying voltage and
 current.

$$v(t) = \frac{1}{C} \int_0^t i(t) dt + V_0$$

Circuit parameters

- The amount of charge stored, $q = CV$.
- C is capacitance in Farad, ratio of the charge on one plate to the voltage difference between the plates. But it does not depend on q or V but capacitor's physical dimensions i.e.,

$$C = \frac{\epsilon A}{d}$$


ϵ = permeability of dielectric in
Wb/Am

A = surface area of plates in m^2


d = distance between the plates
 m



$$R_{eq} = R_1 + R_2$$


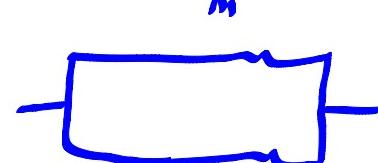

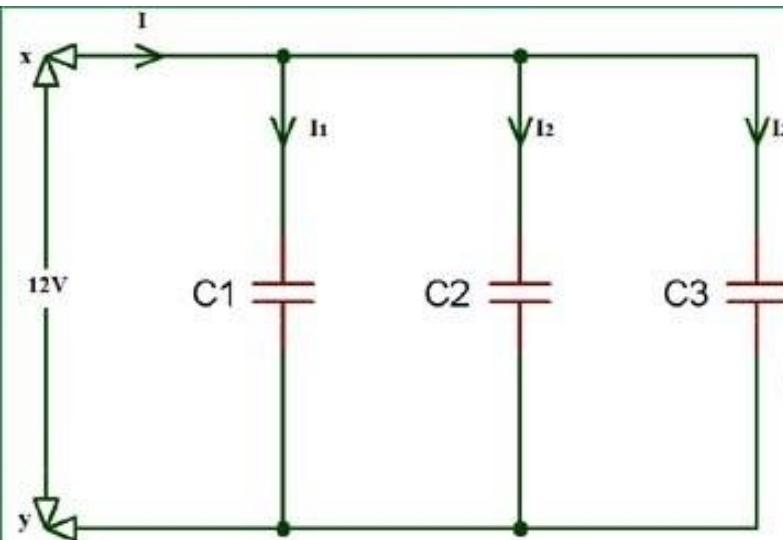
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



Capacitor in Parallel

$$C = C_1 + C_2 + C_3 + \dots + C_n$$

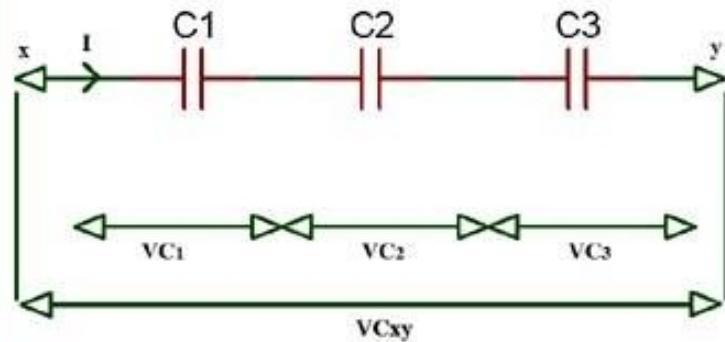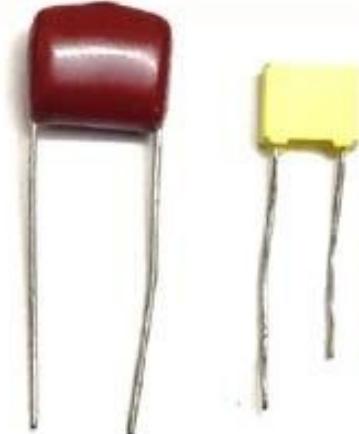

Capacitor in Series

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}$$



Example 2.15

Determine the values of capacitance obtainable by connecting three capacitors (of $5\ \mu\text{F}$, $10\ \mu\text{F}$ and $20\ \mu\text{F}$) (1) in series, (2) in parallel and (3) in series-parallel.

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{5} + \frac{1}{10} + \frac{1}{20}$$

Solution

$$1/\left(\frac{1}{5}, \frac{1}{10}, \frac{1}{20}\right)$$

Let the capacitors of $5\ \mu\text{F}$, $10\ \mu\text{F}$ and $20\ \mu\text{F}$ be C_1 , C_2 , and C_3 , respectively.

1 From Equation (2.24) the equivalent capacitance is the reciprocal of $(1/C_1 + 1/C_2 + 1/C_3)$ i.e.

$$1/[(1/5) + (1/10) + (1/20)] = 1/[0.2 + 0.1 + 0.05] = 1/0.35 = 2.86\ \mu\text{F}$$

2 From Equation (2.25) the equivalent capacitance is

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad C_1 = 5 \mu\text{F} \quad C_2 = 10 \mu\text{F} \quad C_3 = 20 \mu\text{F}$$

3 (a) When C_1 is connected in series with the parallel combination of C_2 and C_3 , the equivalent capacitance is the reciprocal of

$$[1/C_1 + 1/(C_2 + C_3)] = 1/[1/5 + 1/30] = 1/[0.2 + 0.033] = 4.29 \mu\text{F}$$

(b) Similarly when C_2 is in series with the parallel combination of C_3 and C_1 the equivalent capacitance is


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_3} \Rightarrow C_{eq} = 1 / \left(\frac{1}{C_1} + \frac{1}{C_3} \right)$$

$$1/[1/10 + 1/20] = 1/[0.1 + 0.05] = 1/0.15 = 6.67 \mu\text{F}$$

(c) Similarly when C_3 is in series with the parallel combination of C_1 and C_2 the equivalent capacitance is

$$1/[1/20 + 1/10] = 1/[0.05 + 0.1] = 1/0.15 = 6.67 \mu\text{F}$$


INDUCTOR

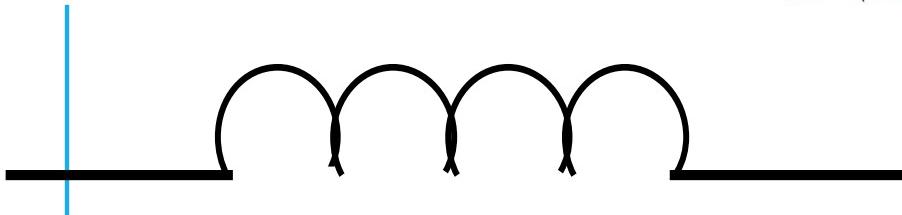

L

UNIT: Henry (H)

- Electrical component that opposes any change in electrical current.
- Composed of a coil or wire wound around a non-magnetic core/magnetic core.
- Its behavior based on phenomenon associated with magnetic fields, which the source is current.
- A time-varying magnetic fields induce voltage in any conductor linked by the fields.
- Inductance is the circuit parameter which relates the induced voltage to the current.

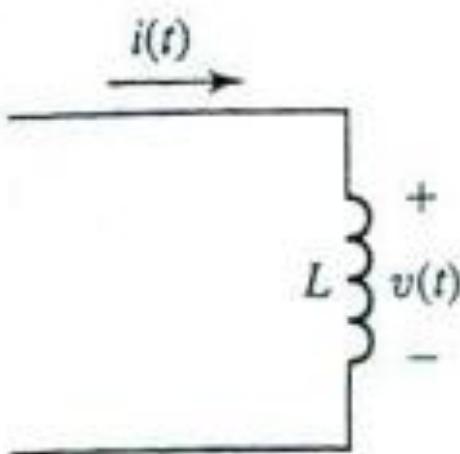


$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$$

FIGURE 3–2
 Inductance with instantaneous time-varying voltage and current.


$$i(t) = \frac{1}{L} \int_0^t v(t) dt + I_0$$

TYPICAL FORM OF AN INDUCTOR

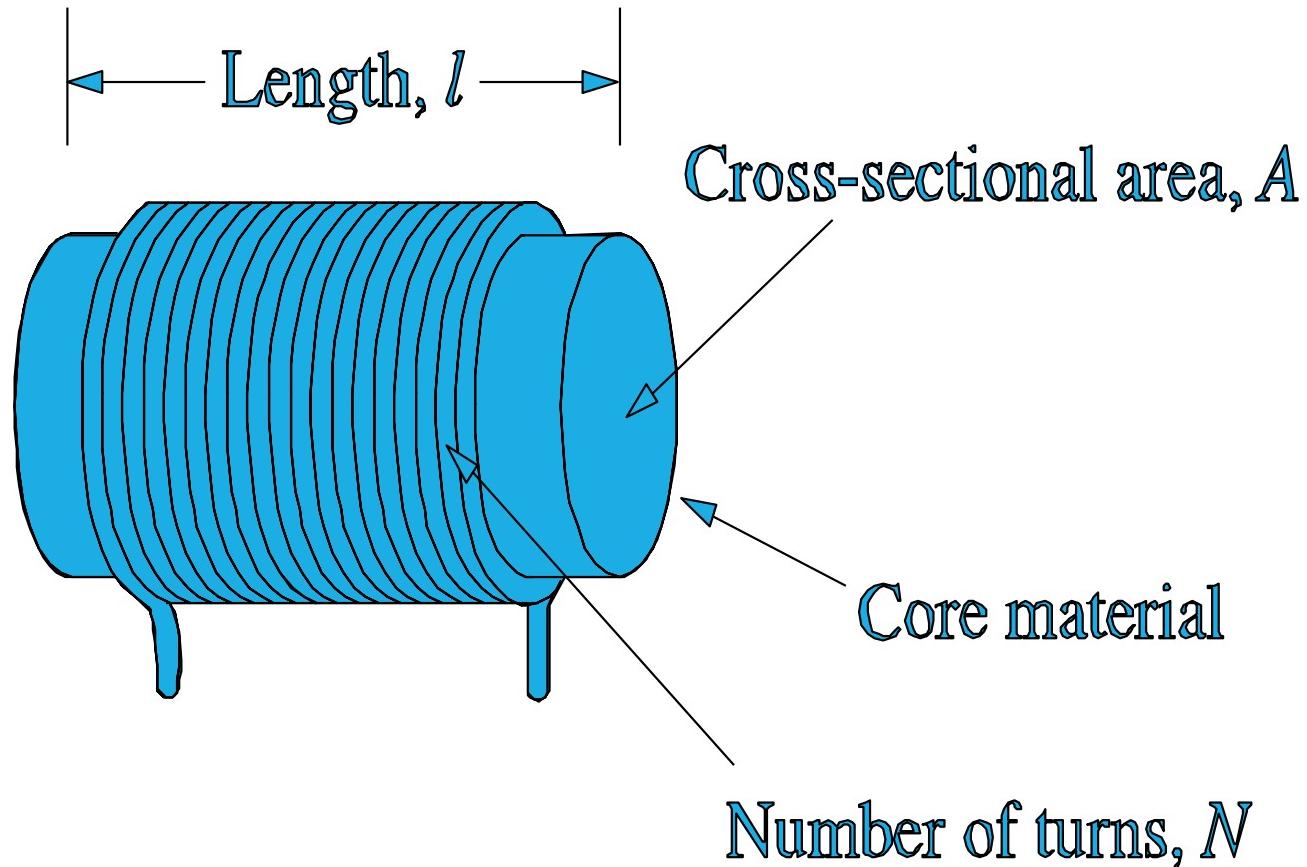





CIRCUIT SYMBOLS FOR INDUCTORS

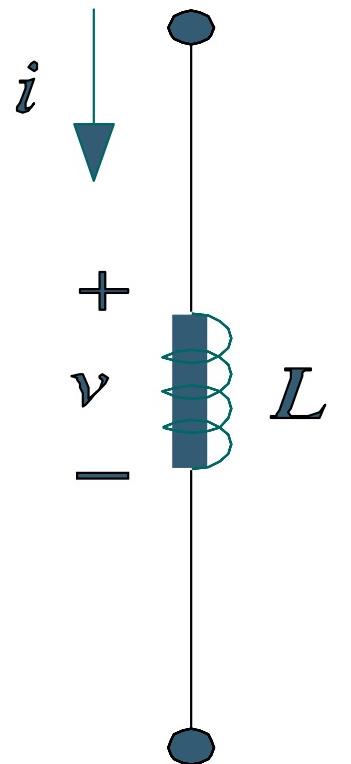

(a)

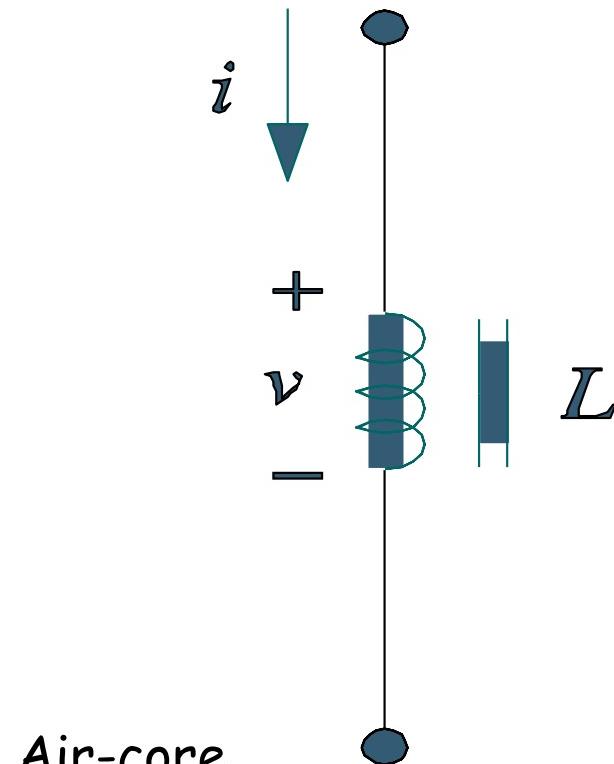



(b)

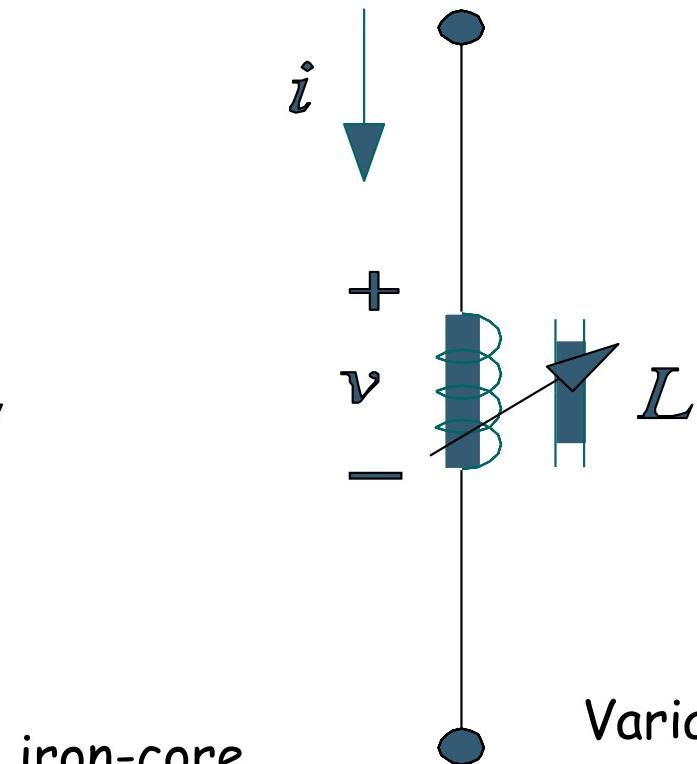

(c)

Variable
iron-core

INDUCTORS IN SERIES AND PARALLEL

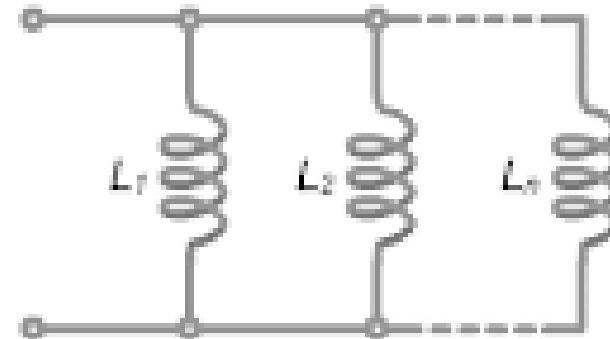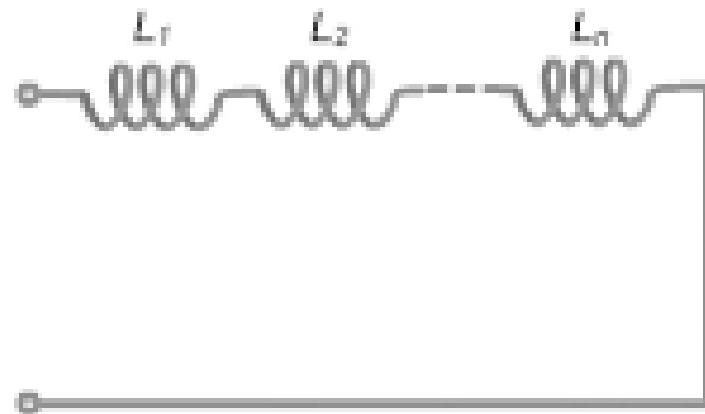

$$L_T = L_1 + L_2 + L_3 + \dots + L_n$$

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

Elements	RESISTOR	CAPACITOR	INDUCTOR
Symbol			
Denoted by	R	C	L
Equation	$R = \frac{V}{I}$	$C = \frac{Q}{V}$	$L = \frac{V_L}{(di/dt)}$
Series	$R_T = R_1 + R_2$	$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$	$L_T = L_1 + L_2$
Parallel	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$	$C_T = C_1 + C_2$	$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2}$