



مدرس خصوصى



اونلاين

يحصل الطالب على ...

\* مقاطع فيديو هات لشرح المقرر بشكل وافي

\* ملخص للمادة للمراجعة النهائية

\* محاضرات مباشرة على برنامج Zoom

\* تواصل مستمر مع معلم المادة للمناقشة

للتواصل



00201024041097






00201096019763

[Mrahmedmahdy.com](http://Mrahmedmahdy.com)
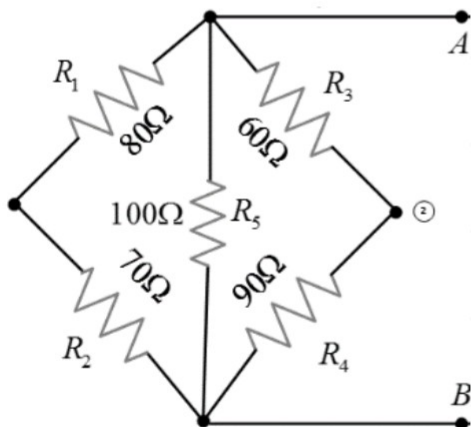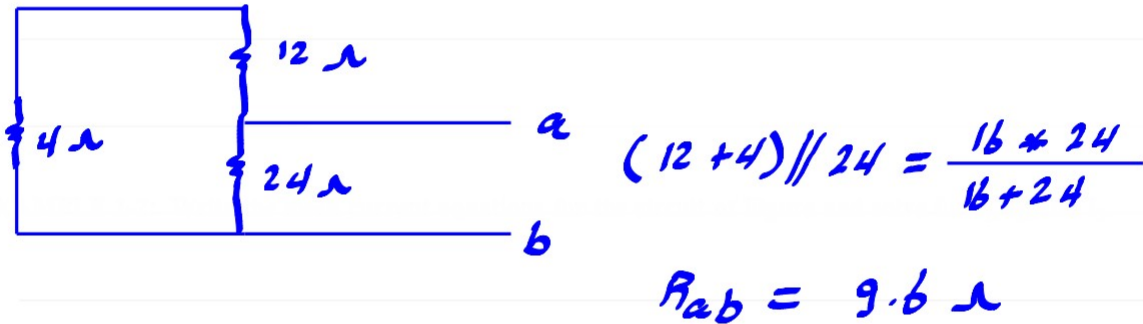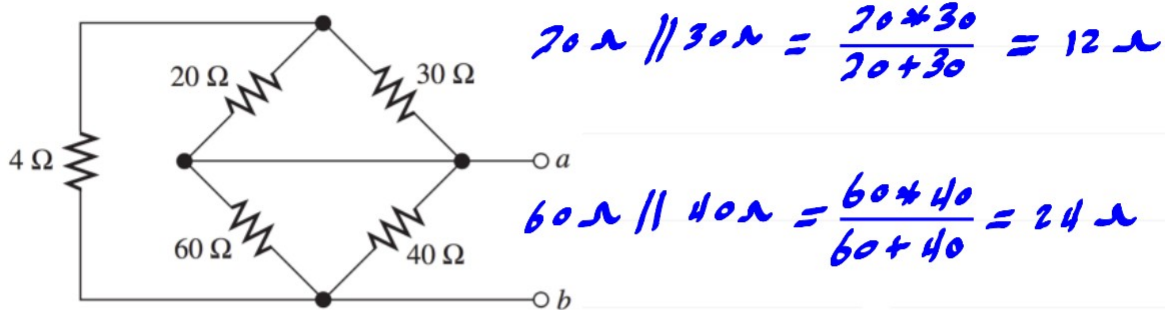
## Assignment #2 – AE 232

1- Find the equivalent resistance at terminals a and b.



$(R_1 + R_2) \parallel R_5 \parallel (R_3 + R_4)$   
 $(80 + 70) \parallel 100 \parallel (60 + 90)$


$R_{AB} = \frac{1}{\frac{1}{150} + \frac{1}{100} + \frac{1}{150}} = 42.86\ \Omega$



2-

Find the current  $i_L$  in the circuit shown on the left, using the node voltage method.

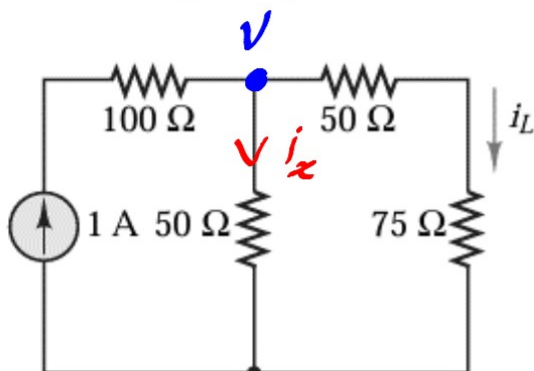Find the voltage  $v_x$  by the node voltage method for the circuit shown on the right.



apply N.V.M


$$1 = I_x + I_L$$

$$1 = \frac{V}{50} + \frac{V}{50+75}$$

$$250 = 5V + 2V$$

$$V = 35.71V$$

$$i_L = \frac{35.71}{50+75} = 0.2777A$$

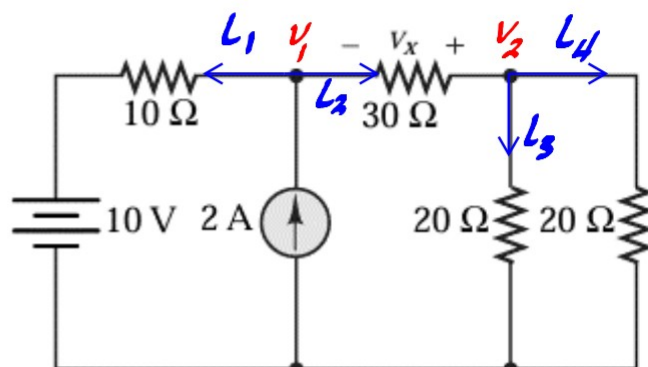

apply N.V.M at node 1

$$-I_1 + 2 - I_2 = 0$$

$$-\frac{V_1 - 10}{10} + 2 - \frac{V_1 - V_2}{30} = 0 \quad \times 30$$

$$-3V_1 + 30 + 60 - V_1 + V_2 = 0$$

$$-4V_1 + V_2 = -90 \rightarrow \textcircled{1}$$

apply N.V.M at node 2

$$I_2 - I_3 - I_4 = 0$$

$$\frac{V_1 - V_2}{30} - \frac{V_2}{20} - \frac{V_2}{20} = 0 \quad \times 60$$

$$2V_1 - 8V_2 = 0 \rightarrow \textcircled{2}$$


$$V_1 = 24V, V_2 = 6V$$

$$V_x = V_2 - V_1 = 6 - 24 = -18V$$

### EXAMPLE 3.5
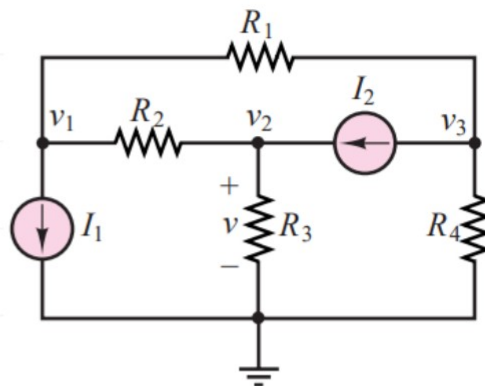
#### Problem

Use the node voltage analysis to determine the voltage  $v$  in the circuit of Figure 3.9. Assume that  $R_1 = 2\ \Omega$ ,  $R_2 = 1\ \Omega$ ,  $R_3 = 4\ \Omega$ ,  $R_4 = 3\ \Omega$ ,  $I_1 = 2\text{ A}$ , and  $I_2 = 3\text{ A}$ .



Repeat the exercise of Example 3.5 when the direction of the current sources becomes the opposite. Find  $v$ .

Answer:  $v = 0.4\text{ V}$

apply N.V.M at node 1

$$2 - I_1 - I_2 = 0$$

$$2 - \frac{v_1 - v_2}{1} - \frac{v_1 - v_3}{2} = 0$$

$$-3v_1 + 2v_2 + v_3 = -4 \rightarrow \textcircled{1}$$

apply N.V.M at node 2


$$I_1 - I_3 - 3 = 0$$

$$\frac{v_1 - v_2}{1} - \frac{v_2}{4} - 3 = 0$$

$$4v_1 - 5v_2 = 12 \rightarrow \textcircled{2}$$

apply N.V.M at node 3

$$I_2 + 3 - I_4 = 0$$

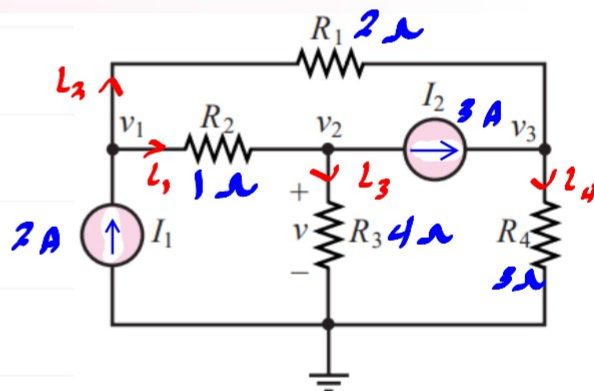

$$\frac{v_1 - v_2}{2} + 3 - \frac{v_3}{3} = 0$$

$$3v_1 - 5v_3 = -18 \rightarrow \textcircled{3}$$

$$v_1 = 3.5\text{ V}, v_2 = 0.4\text{ V}$$


$$v_3 = 5.7\text{ V}$$

$$v = v_2 = 0.4\text{ V}$$

### EXAMPLE 3.6

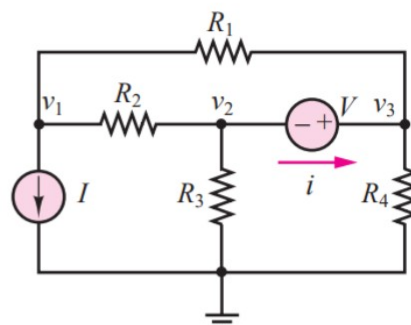
#### Problem

Use node analysis to determine the current  $i$  flowing through the voltage source in the circuit of Figure 3.11. Assume that  $R_1 = 2\ \Omega$ ,  $R_2 = 2\ \Omega$ ,  $R_3 = 4\ \Omega$ ,  $R_4 = 3\ \Omega$ ,  $I = 2\text{ A}$ , and  $V = 3\text{ V}$ .



Repeat the exercise of Example 3.6 when the direction of the current source becomes the opposite. Find the node voltages and  $i$ .

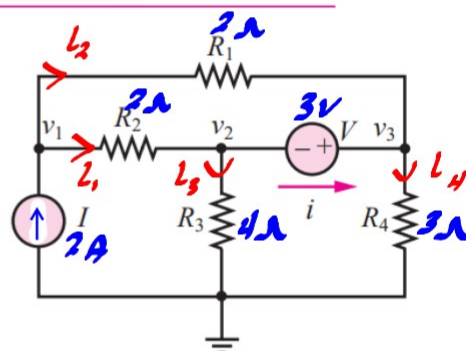Answer:  $v_1 = 5.21\text{ V}$ ,  $v_2 = 1.71\text{ V}$ ,  $v_3 = 4.71\text{ V}$ , and  $i = 1.32\text{ A}$



$$v_3 - v_2 = 3 \Rightarrow \text{super node}$$

$$-v_2 + v_3 = 3 \rightarrow \textcircled{1}$$

apply N.V.M at node 1

$$2 - L_1 - L_2 = 0 \Rightarrow 2 - \frac{v_1 - v_2}{2} - \frac{v_1 - v_3}{2} = 0$$

$$-2v_1 + v_2 + v_3 = -4 \rightarrow \textcircled{2}$$

apply N.V.M at node ②

$$L_1 - L_3 - L = 0 \Rightarrow \frac{v_1 - v_2}{2} - \frac{v_2}{4} - L = 0$$

$$2v_1 - 3v_2 - 4L = 0 \rightarrow \textcircled{3}$$

apply N.V.M at node ③


$$L_2 + L - L_4 = 0 \Rightarrow \frac{v_1 - v_3}{2} + L - \frac{v_3}{3} = 0$$

$$3v_1 - 5v_3 + 6L = 0 \rightarrow \textcircled{4}$$

$$v_1 = \frac{73}{14}\text{ V}, v_2 = \frac{12}{7}\text{ V}, v_3 = \frac{33}{7}\text{ V}, L = \frac{37}{28}\text{ A}$$



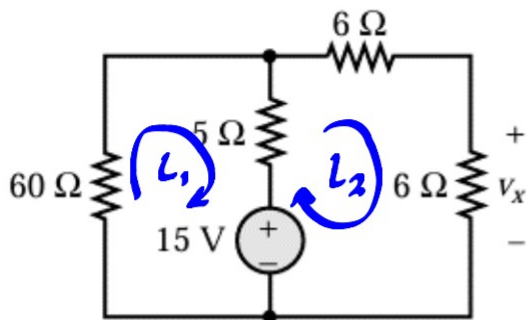- 5- Find the unknown voltage  $v_x$  by mesh current analysis in the circuit on the left.  
Find the unknown current  $I_x$ , using the mesh current method in the circuit on the right.



apply M.C.M at mesh 1

$$60I_1 + 5(I_1 - I_2) + 15 = 0$$

$$65I_1 - 5I_2 = -15 \rightarrow \textcircled{1}$$

apply M.C.M at mesh 2


$$-15 + 5(I_2 - I_1) + 6I_2 + 6I_2 = 0$$

$$-5I_1 + 17I_2 = 15 \rightarrow \textcircled{2}$$

$$I_1 = -0.1667 \text{ A} = -166.7 \text{ mA}$$

$$I_2 = 0.8333 \text{ A} = 833.3 \text{ mA}$$

$$V_x = 6 \times 0.8333 = 5 \text{ V}$$

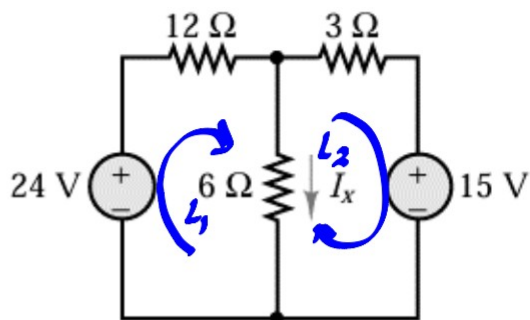

apply M.C.M at mesh 1

$$-24 + 12I_1 + 6(I_1 - I_2) = 0$$

$$18I_1 - 6I_2 = 24 \rightarrow \textcircled{1}$$

apply M.C.M at mesh 2

$$6(I_2 - I_1) + 3I_2 + 15 = 0$$

$$-6I_1 + 9I_2 = -15 \rightarrow \textcircled{2}$$

$$I_1 = 1 \text{ A}$$

$$I_2 = -1 \text{ A}$$

$$I_x = I_1 - I_2 = 2 \text{ A}$$